



Bandgap Reference Circuit

- Shirazush Salekin Chowdhury
 - PhD Student
 - Bradley Department of Electrical and Computer Engineering
 - Virginia Tech
-

What you can learn


- Note: For optimal viewing experience, please use slideshow mode.

Bandgap Reference (BGR)

- BGR generates a fixed DC reference voltage that does not change with the variation of PVT (Process, Supply Voltage, and Temperature) variation
- Application:

- Almost everywhere!
 - ADC, DAC,
 - LDO, Sensors,
 - Oscillators (VCO),
 - Precision Analog Circuits and many more!!

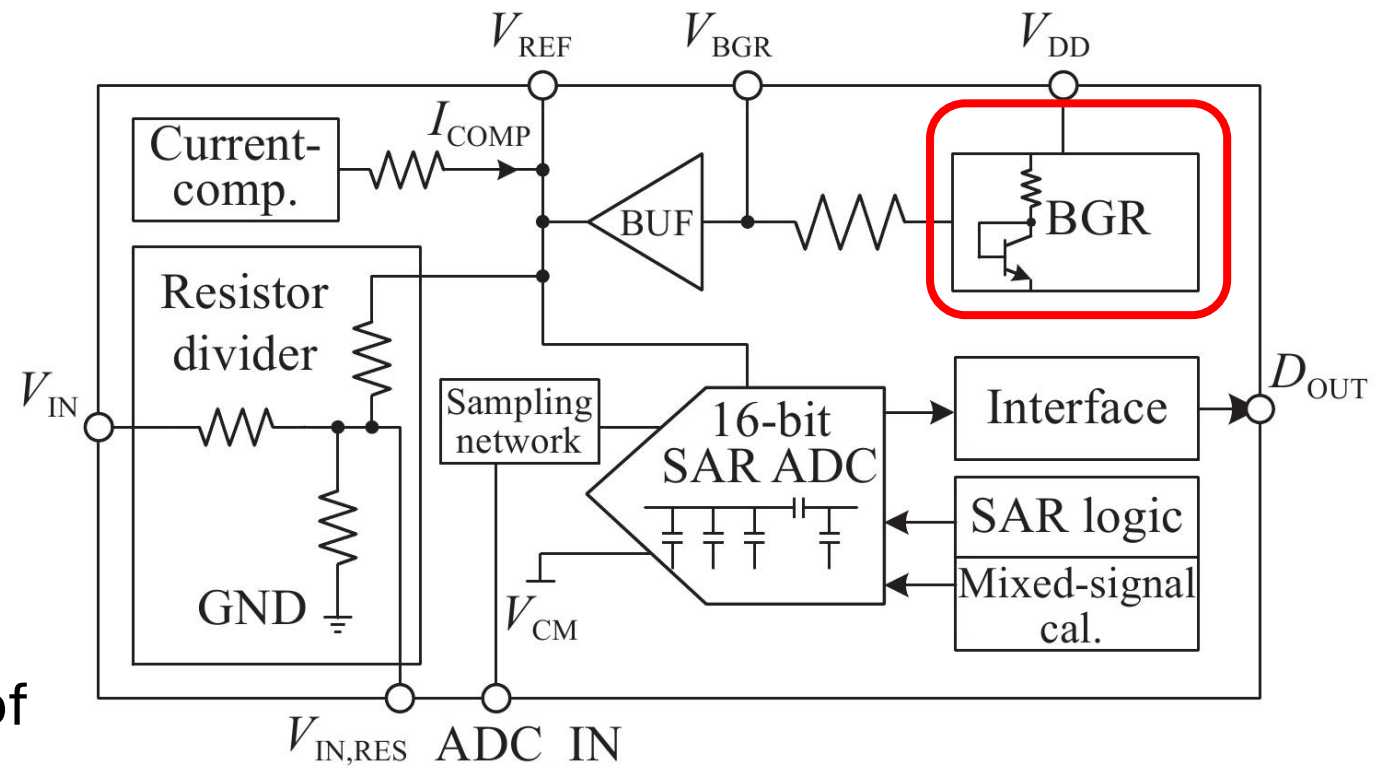Target: Generate a fixed DC voltage proportional to the Bandgap voltage of silicon.



Bandgap Reference Circuit


- The principle of the bandgap voltage reference
 - Balance the negative temperature coefficient of a pn junction with the positive temperature coefficient of the thermal voltage, $V_t = kT/q$.
 - In short → Balance V_{BE} with V_T

- Result

- Provides “almost” constant voltage across different PVT: $V_{BG} \approx 1.2\text{ V}$


- PVT

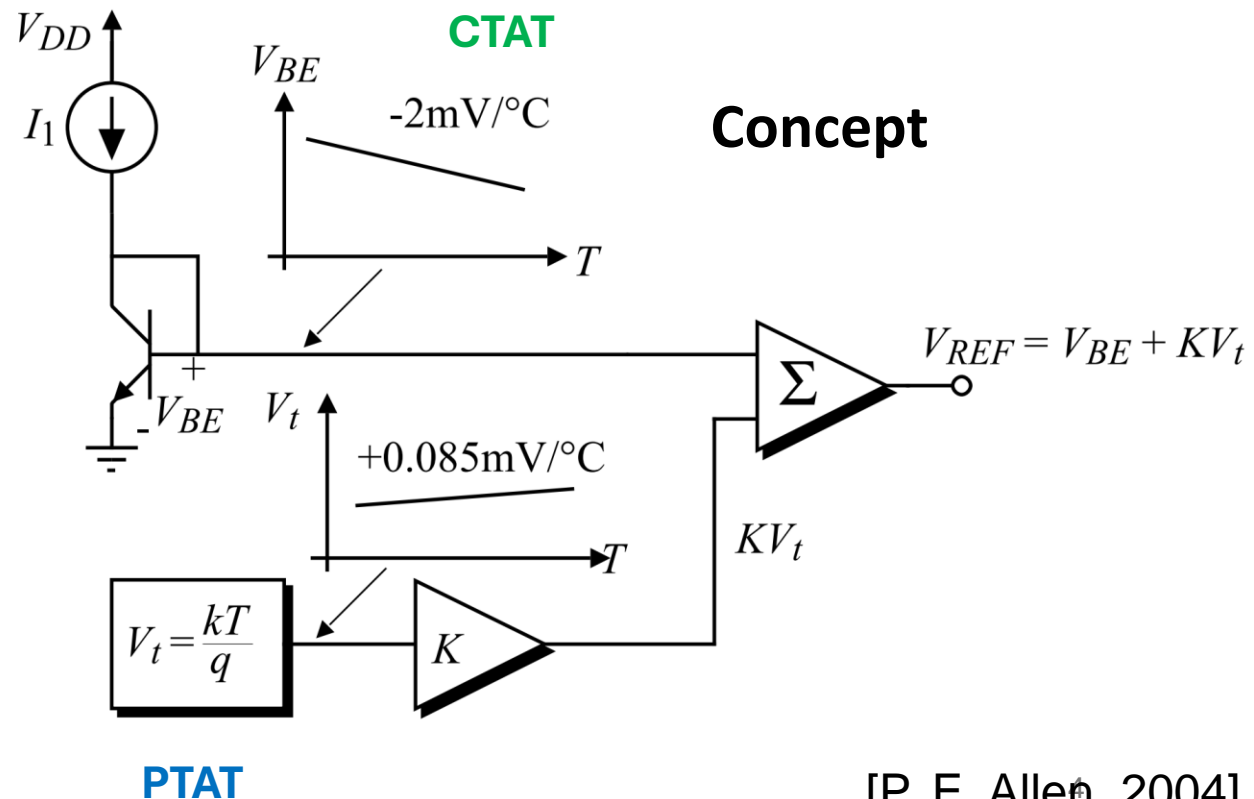- Process, Voltage and Temperature
 - SS_1P62_M40C
 - TT_1P80_25C
 - FF_1P98_125C





Effect of Temperature

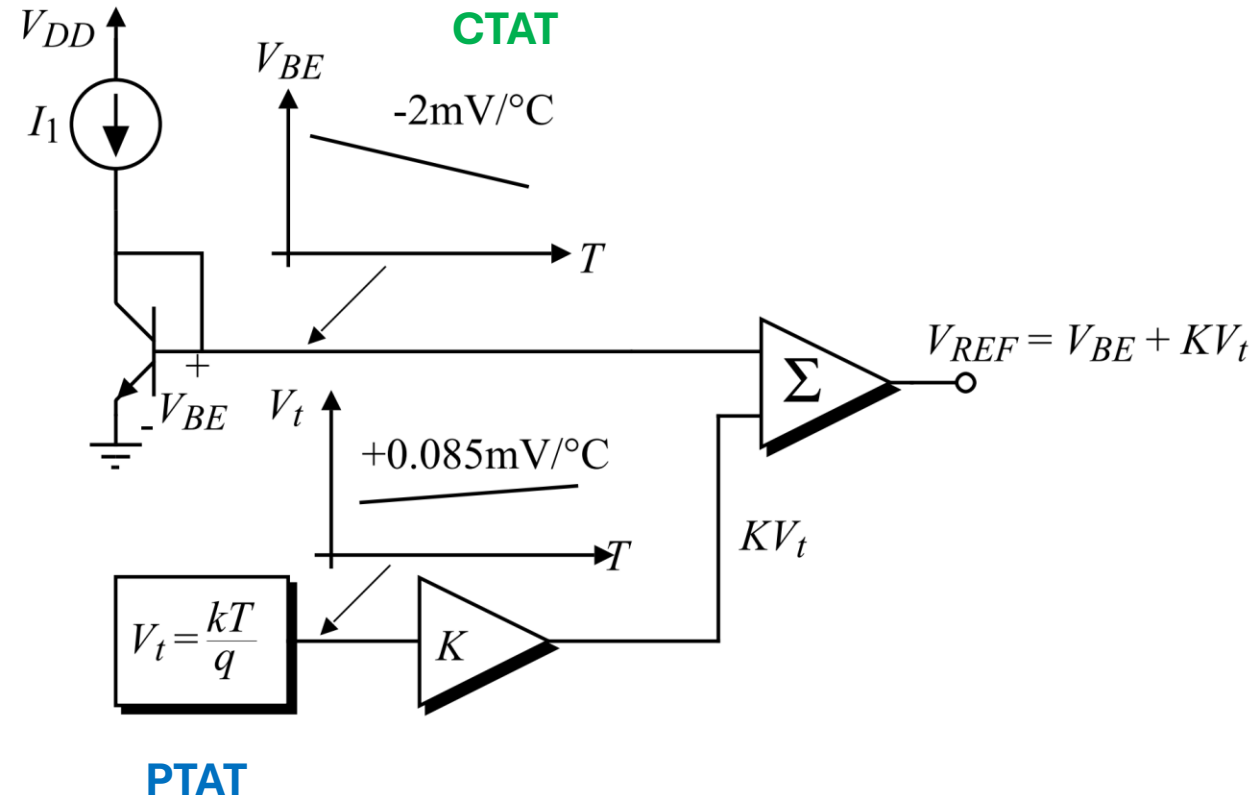- Two voltages,
 - One that increases proportionately with temperature and is called proportional to absolute temperature or PTAT.
 - One that decreases proportionately with temperature and is called complementary to absolute temperature or CTAT.



Effect of Temperature

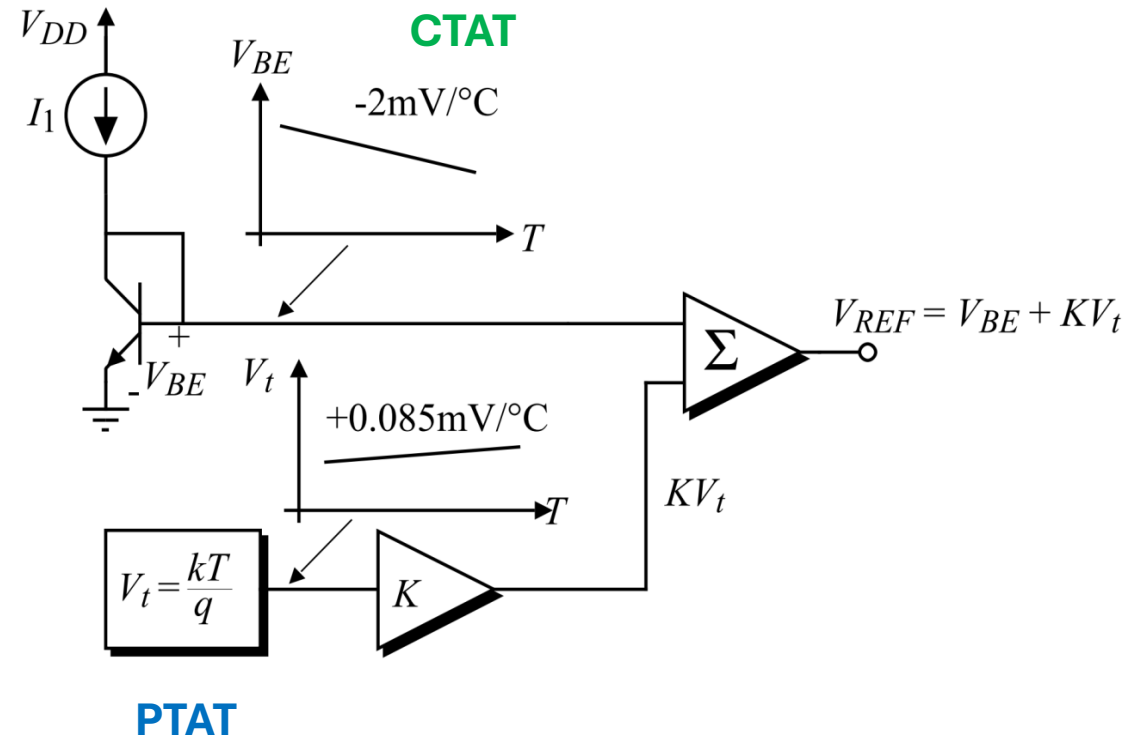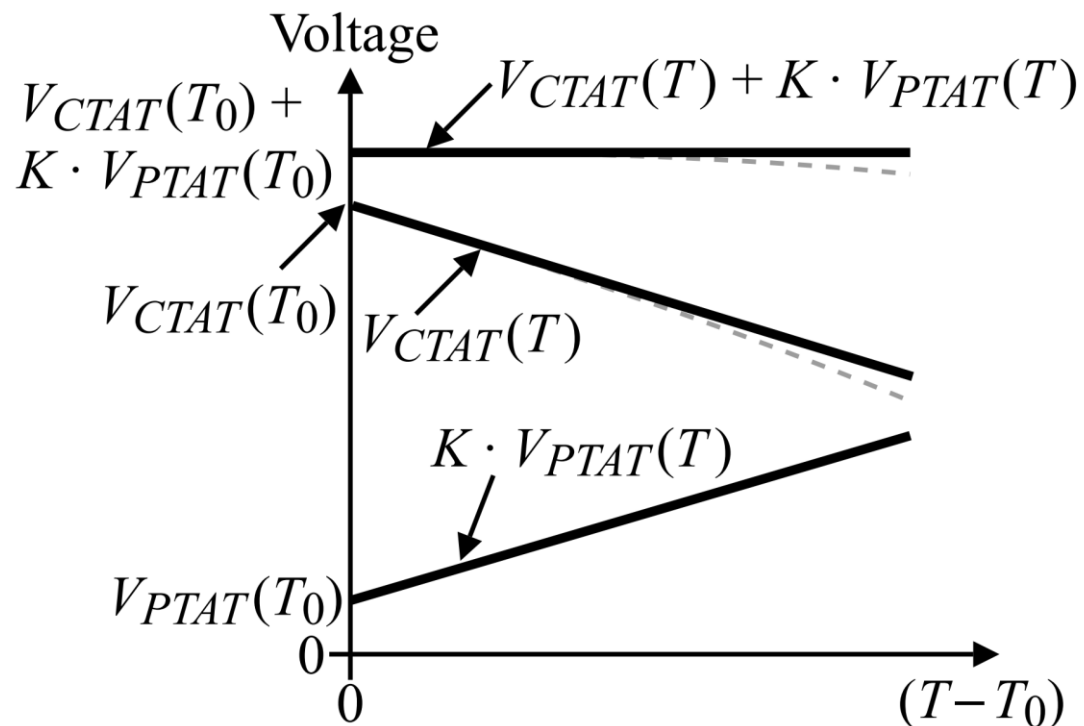- Two voltages,
 - PTAT
 - CTAT
- $ZTC(T) = K \cdot PTAT(T) + CTAT(T)$






[P. E. Allen, 2004]

But HOW!!

- Let's see the basic Bandgap Circuit Structure
- Let's brush up some concepts
 - “Floating” Current Mirror and “Floater”
 - “Virtual Short” of an OpAmp
 - BJT base-emitter voltage
 - KVL and KCL

Basic Bandgap Circuit

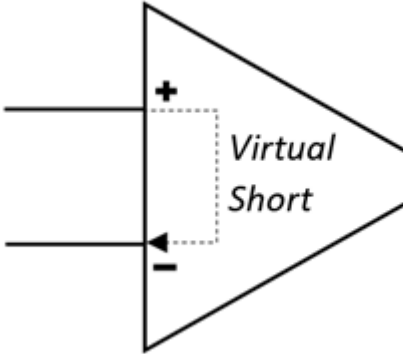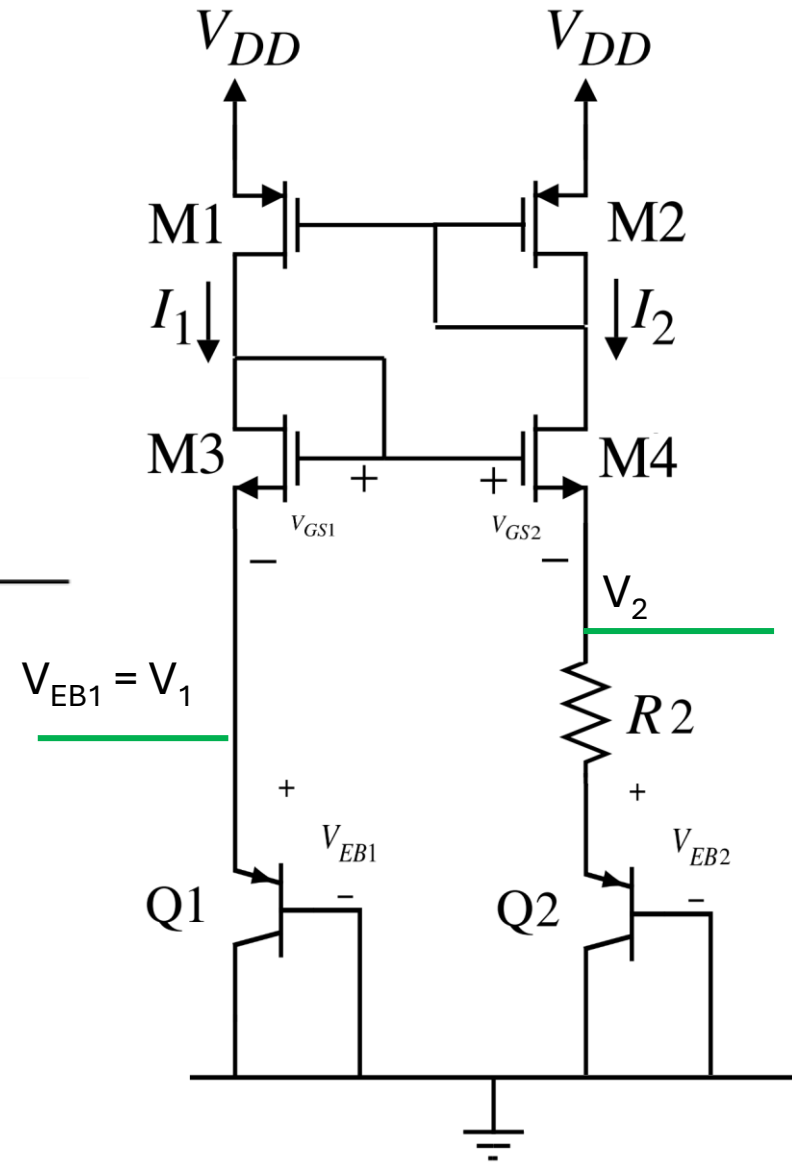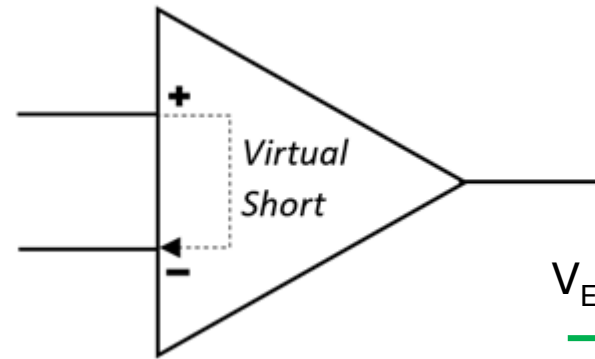- For the BGR to work
 - $V_1 = V_2$
 - How can we make two node voltages equal?
 - Using OpAmp
 - Virtual Short
 - Virtual Ground
 - Asymptotic Equality Principle
 - Using Floating Current Mirror
- 



[P. E. Allen, 2004]


Floating Current Mirror and Floater

Let's Discuss Current Mirror

MOSFET Drain Current Equation:

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{Th})^2$$

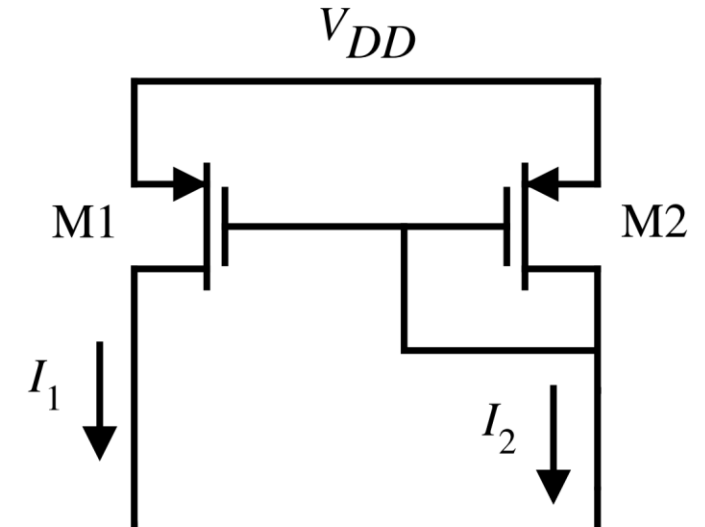- V_{GS} of M1 and M2 are the same.
 - $V_{GS1} = V_{GS2}$
- Both M1 and M2 are *Identical*
 - $I_2 = I_1$



[P. E. Allen, 2004]

In other words, can we force $V1 = V2$?

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{w}{L} (V_{GS} - V_{Th})^2$$

- Since M1, M2, M3 and M4 are *Identical*
 - $I_1 = I_2$
 - $V_{GS1} = V_{GS2}$



Floating Current Mirror and Floater

Are the voltages of V_{GS3} and V_{GS4} equal irrespective of the load?

- Since M1, M2, M3 and M4 are *Identical*

▫ $I_1 = I_2$

$$I_1 = \frac{\mu_n C_{ox}}{2} \frac{w}{L} (V_{GS3} - V_{Th})^2$$

$$I_2 = \frac{\mu_n C_{ox}}{2} \frac{w}{L} (V_{GS4} - V_{Th})^2$$

Since $I_1 = I_2$

$$\frac{\mu_n C_{ox}}{2} \frac{w}{L} (V_{GS3} - V_{Th})^2 = \frac{\mu_n C_{ox}}{2} \frac{w}{L} (V_{GS4} - V_{Th})^2$$


$$(V_{GS3} - V_{Th})^2 = (V_{GS4} - V_{Th})^2$$

$$V_{GS3} = V_{GS4}$$

$$V_{S3} = V_{S4} [\because V_{G3} = V_{G4}]$$




$$V_1 = V_2$$

Floater

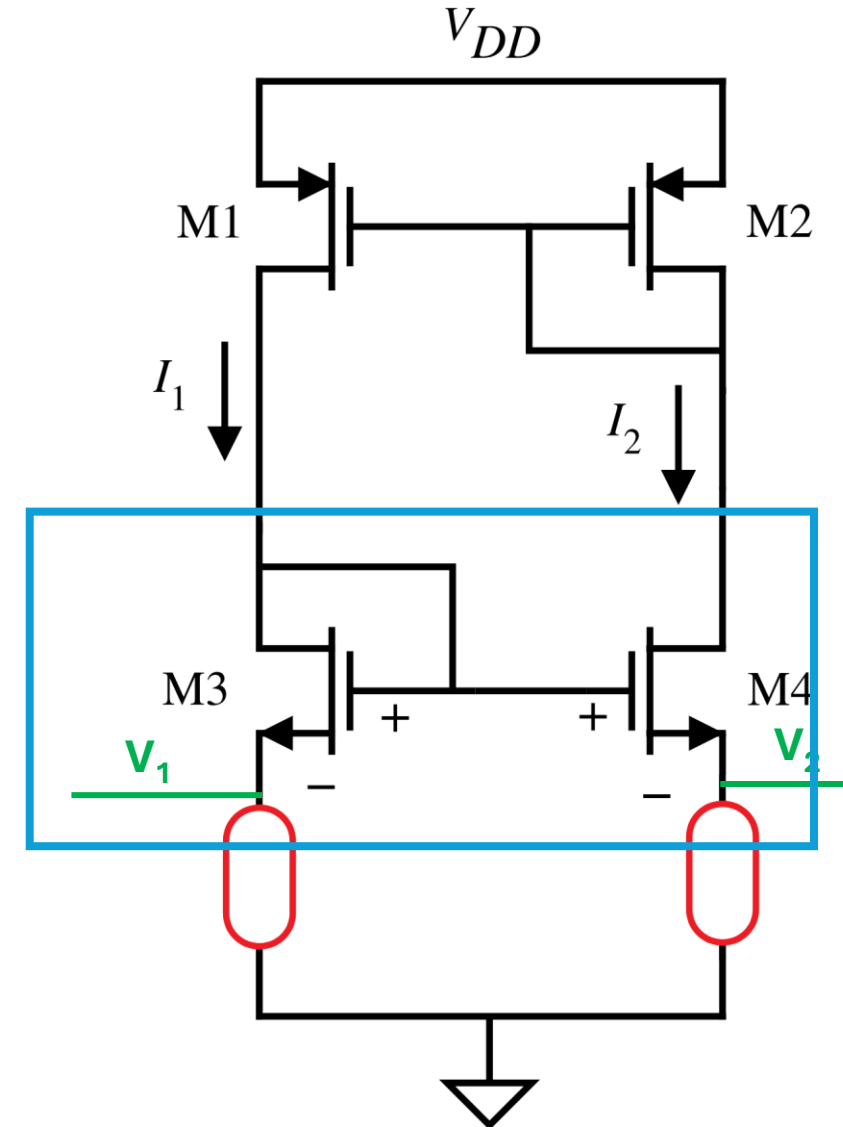

Concept Checkpoint

Note: $V_{DD} = 1.8V$, $V_{SS} = 0V$

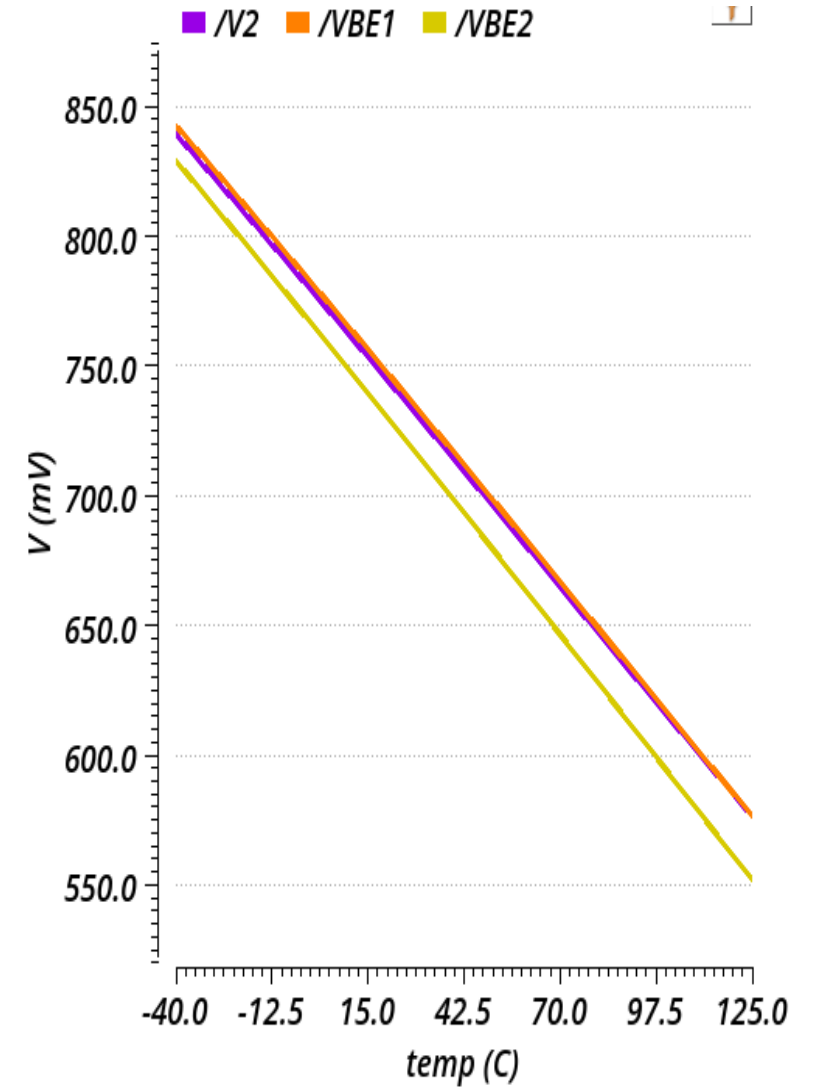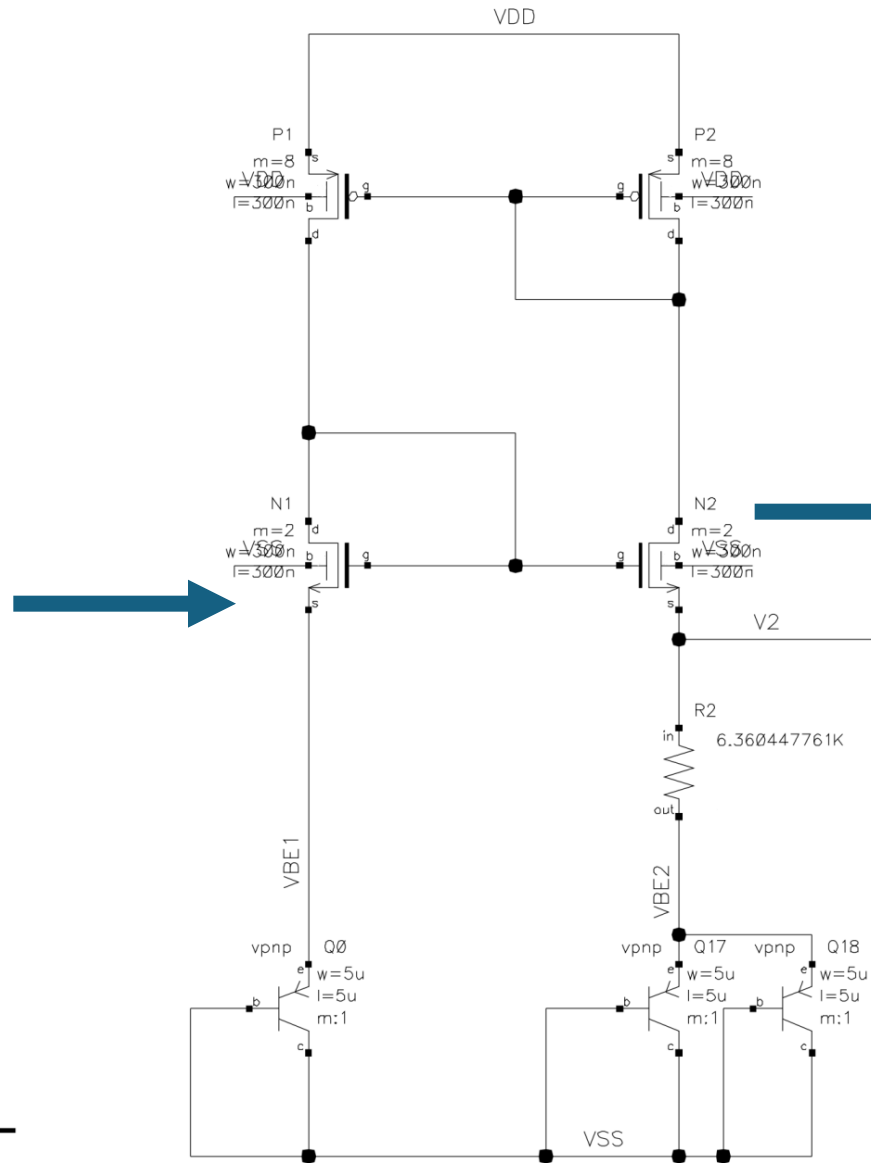
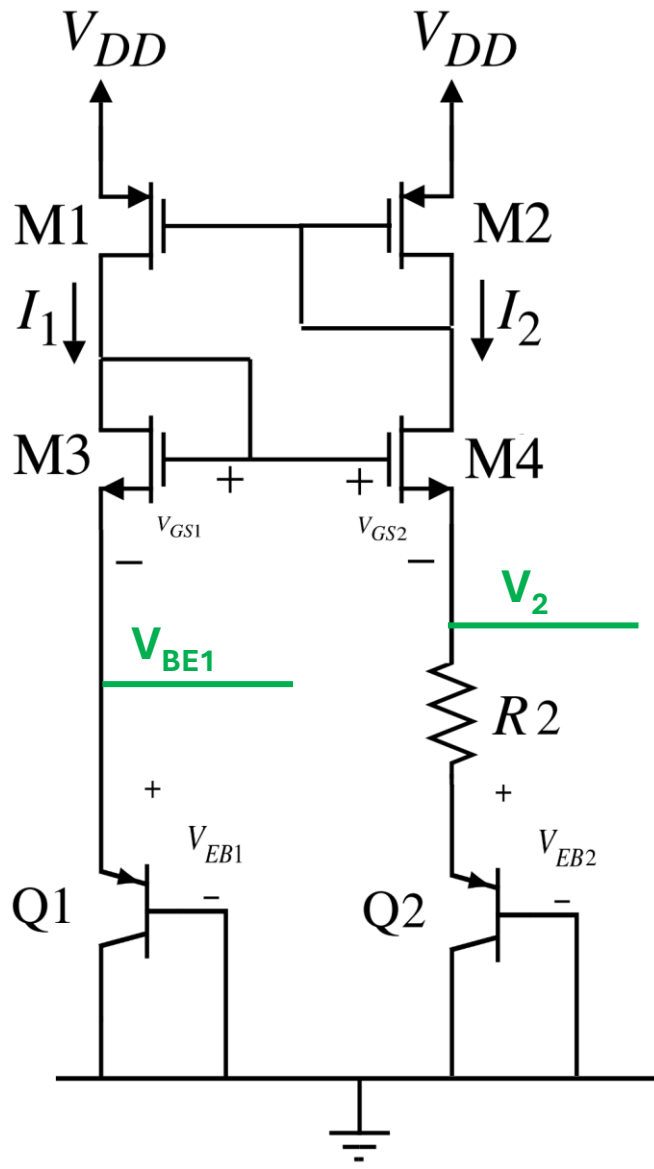


VBE of BJT

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right)$$

$$V_{BE} = \frac{kT}{q} \ln \left(\frac{I_C}{I_S} \right)$$

Isn't $V_{BE} \propto T$??

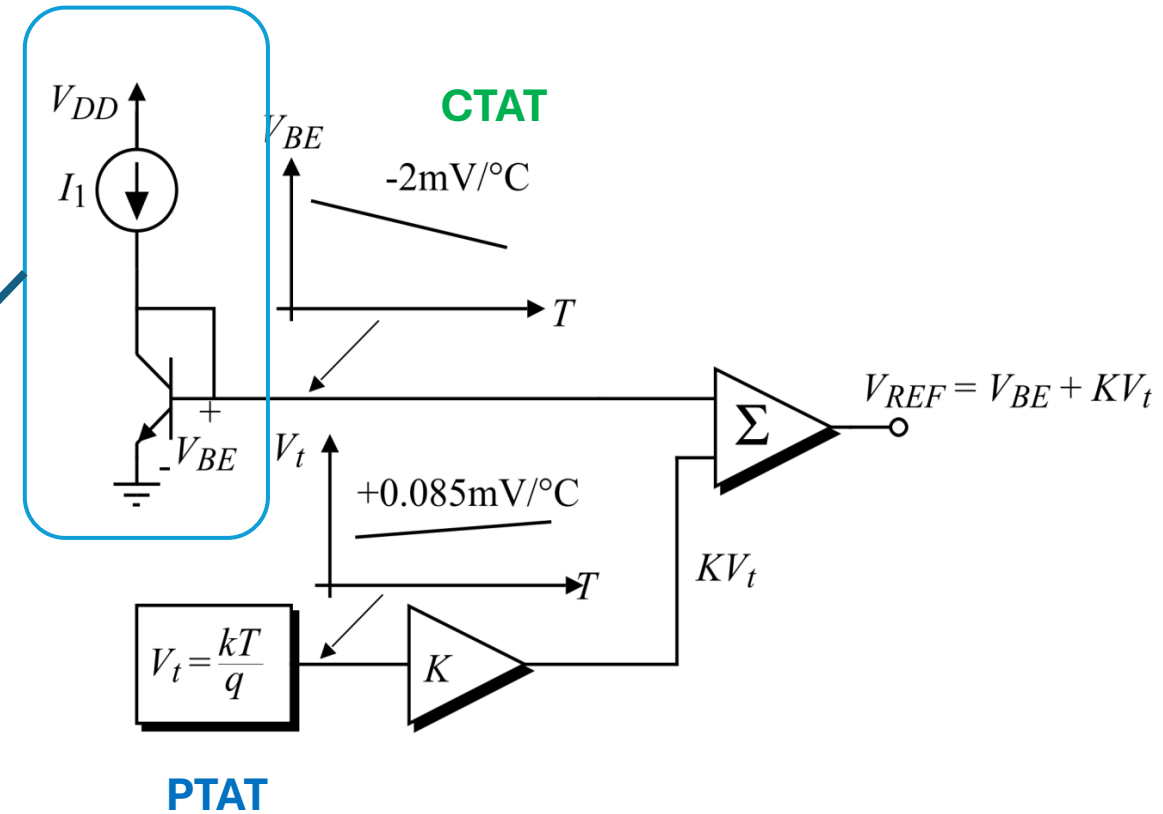
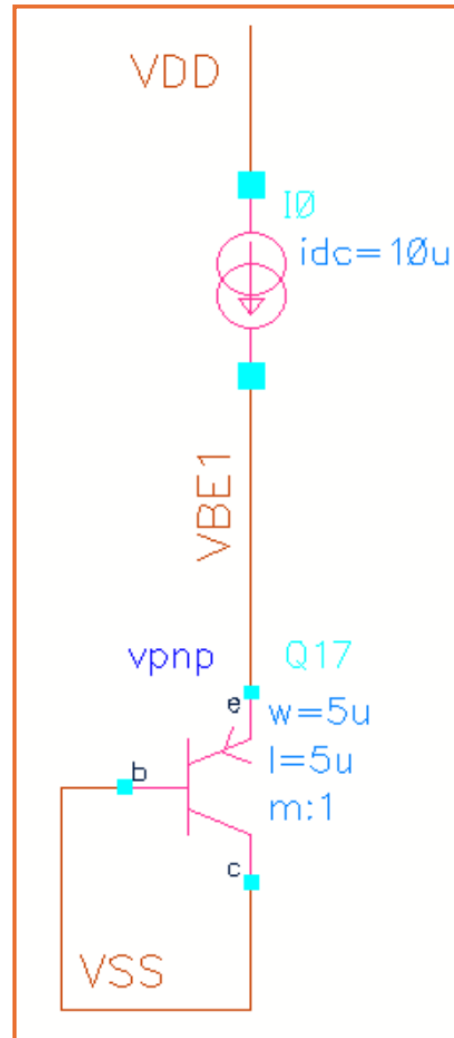


[P. E. Allen, 2004]

Let's Do a simulation!

Sweep the temp from -40°C to 125°C

CTAT Current

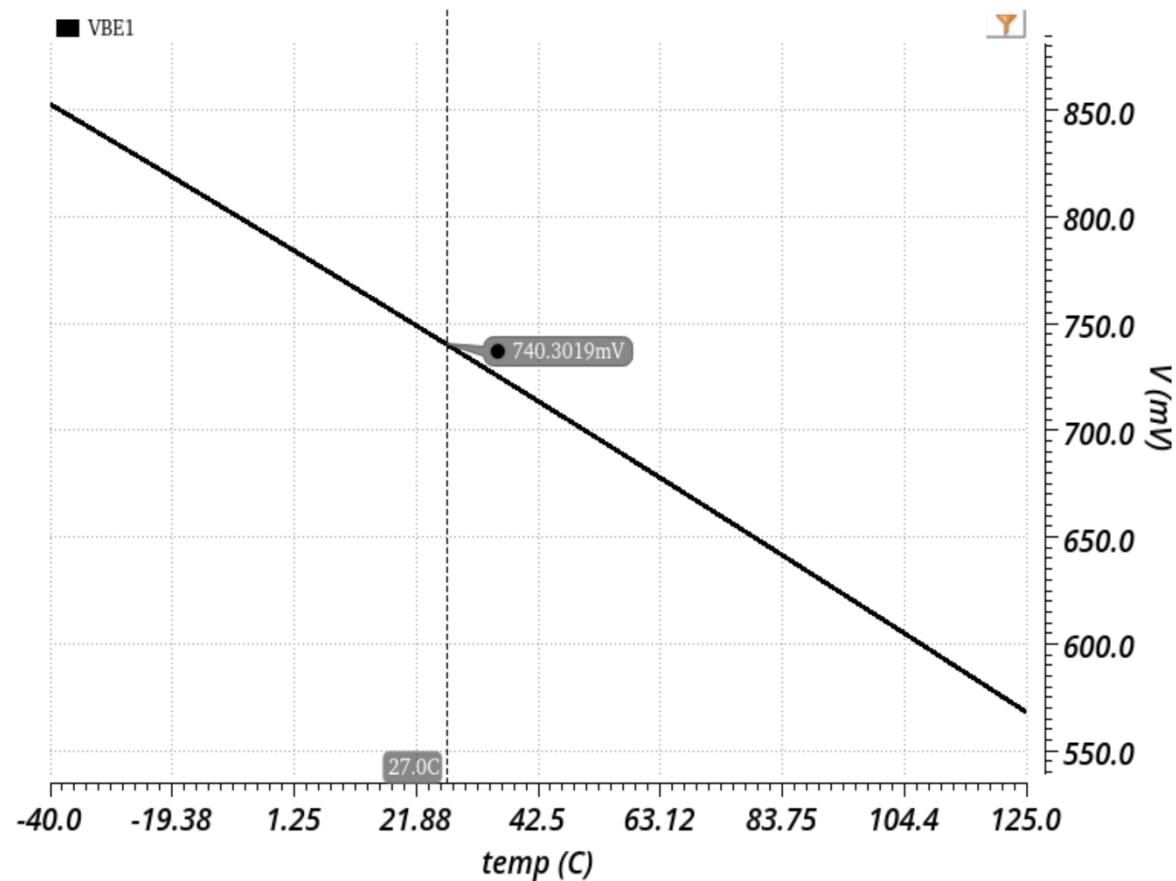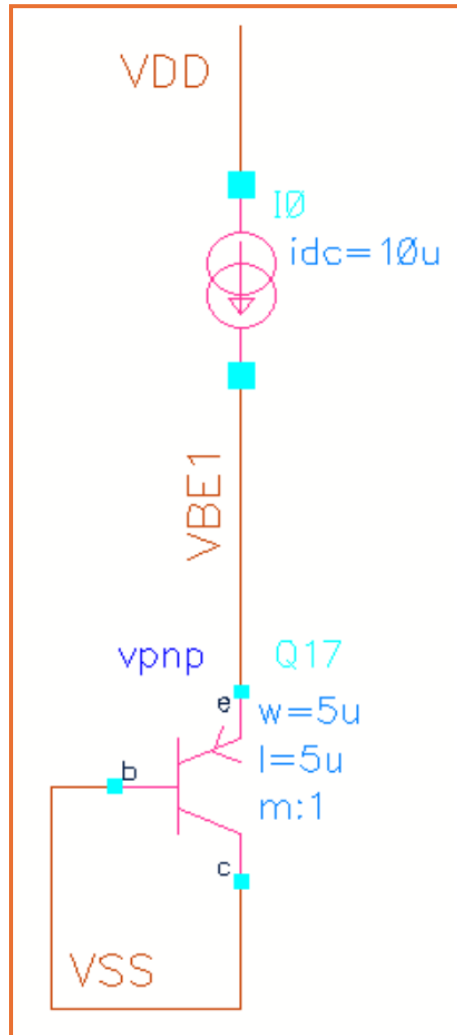

$$V_{BE} = \frac{kT}{q} \ln \left(\frac{I_C}{I_S} \right)$$



Why is the voltage decreasing?

$$V_{BE} = \frac{kT}{q} \ln \left(\frac{I_C}{I_S} \right)$$

VBE of BJT as CTAT


Sweep the temp from -40°C to 125°C

CTAT Current

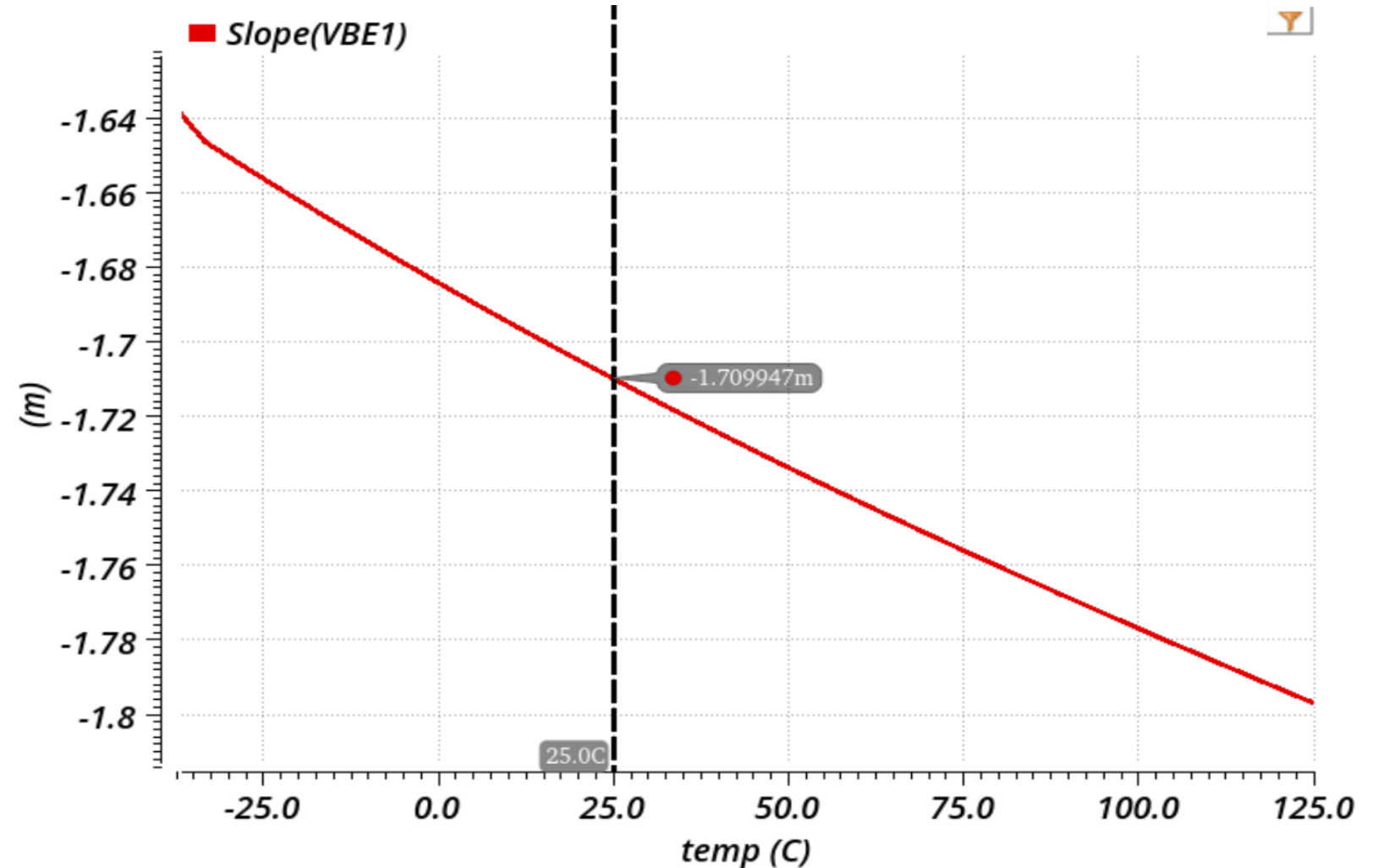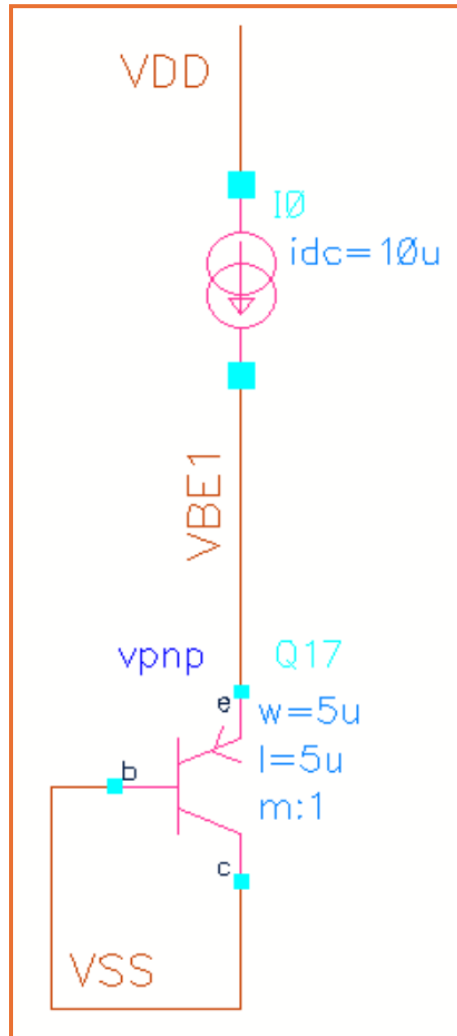

VBE of BJT as CTAT

CTAT Current

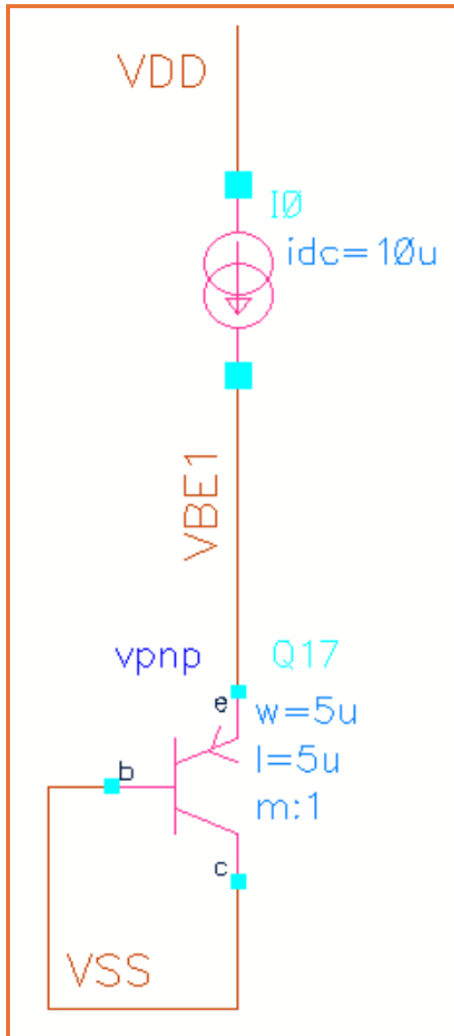

$$V_{BE} = \frac{kT}{q} \ln \left(\frac{I_C}{\boxed{I_S}} \right)$$

- I_S has such an incredibly strong temp dependence that even through the log it overwhelms the proportional Temp dependence!
- Let's see HOW!

VBE of BJT as CTAT

$$V_{BE} = \frac{kT}{q} \ln \left(\frac{I_C}{I_S} \right)$$

I_S = Saturation Current of BJT

$$I_S = \frac{qA n_i^2 D}{WN_A}$$

Where,

q = Electron Charge (Constant)

A = Area of Emitter (Constant at 1st order)

W = Width of Base (Constant at 1st order)

N_A = Doping Concentration (Constant)

D = Diffusion Constant (NOT CONSTANT)

n_i^2 = Number of intrinsic carrier concentration

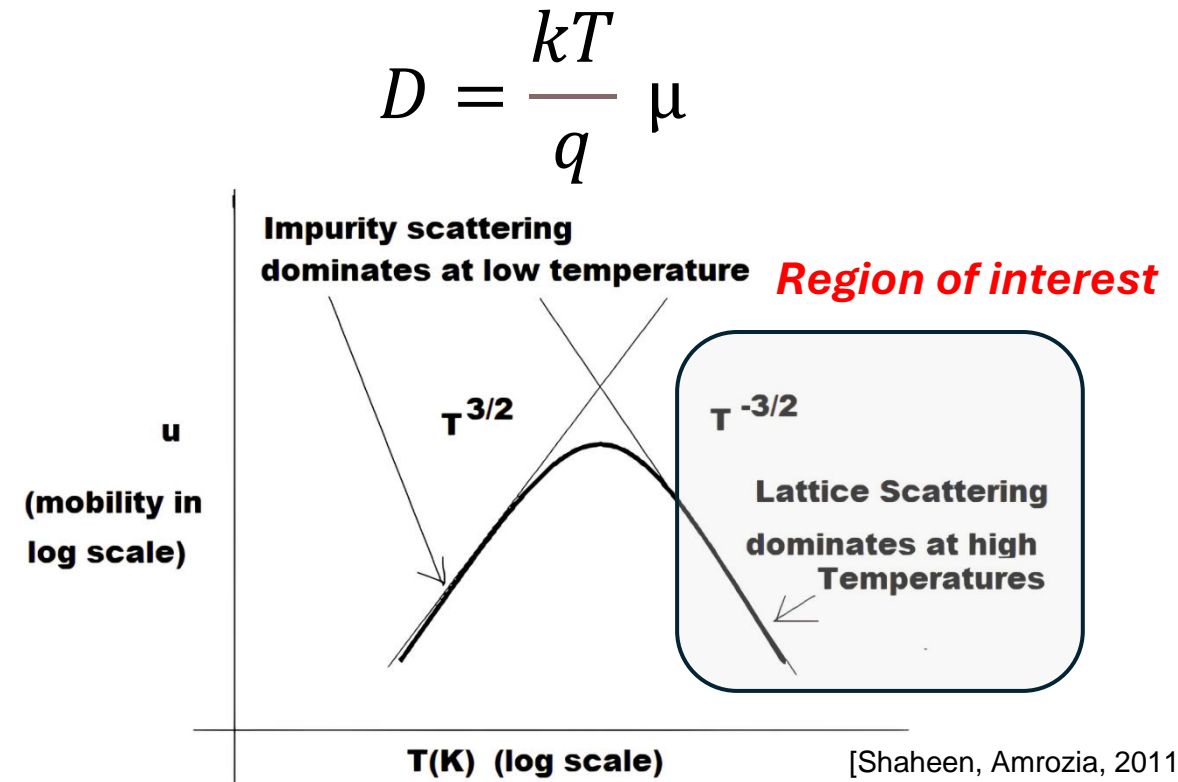


Figure. Temperature dependence of mobility in Si.

$$D = \frac{kT}{q} \mu = \frac{kT}{q} T^{-3/2}$$

$$n_i^2 = D' T^3 e^{-\frac{V_{BG}}{V_T}}$$

VBE of BJT as CTAT

$$V_{BE} = \frac{kT}{q} \ln \left(\frac{I_C}{I_S} \right)$$

$$I_S = \frac{qA n_i^2 D}{WN_A}$$

$$n_i^2 = D' T^3 e^{-\frac{V_{BG}}{V_T}}$$

$$\begin{aligned} D &= \frac{kT}{q} \mu \\ &= \frac{kT}{q} T^{-3/2} \end{aligned}$$

$$I_S = \frac{qA \left(D' T^3 e^{-\frac{V_{BG}}{V_T}} \right) \frac{kT}{q} T^{-3/2}}{WN_A}$$

$$I_S = E \cdot T^3 \cdot T \cdot T^{-\frac{3}{2}} e^{-\frac{V_{BG}}{V_T}}$$

$$I_S = E \cdot T^{\frac{5}{2}} e^{-\frac{V_{BG}}{V_T}}$$

VBE of BJT as CTAT

$$I_S = E \cdot T^{\frac{5}{2}} e^{-\frac{V_{BG}}{V_T}}$$

Can we use MOSFET to achieve CTAT?

No. Since the Electrical Behavior of MOSFET is heavily process Dependent!

$$V_{BE} = \frac{kT}{q} \ln \left(\frac{I_C}{I_S} \right)$$

Overall CTAT

$$V_{BE} = \frac{kT}{q} \ln(I_C) - \frac{kT}{q} \ln(I_S)$$

$$V_{BE} = \frac{kT}{q} \ln(I_C) - \frac{kT}{q} \ln(E) - \frac{5kT}{2q} \ln(T) + \cancel{\frac{kT}{q}} \cdot \cancel{\frac{V_{BG}}{V_T}}$$

$$V_{BE} = \underbrace{\frac{kT}{q} \ln(I_C)}_{\text{Weak PTAT}} - \underbrace{\frac{kT}{q} \ln(E) - \frac{5kT}{2q} \ln(T)}_{\text{Strong CTAT}} + \underbrace{V_{BG}}_{\text{Constant BG voltage}}$$

Weak PTAT

Strong CTAT

Constant BG voltage

Base-Emitter Voltage of BJT

$$V_{BE} = \underbrace{\frac{kT}{q} \ln(I_c)}_{\text{Weak PTAT}} - \underbrace{\frac{kT}{q} \ln(E) - \frac{5kT}{2q} \ln(T)}_{\text{Strong CTAT}} + \underbrace{V_{BG}}_{\text{Constant BG voltage}}$$

- Overall Negative Temp coefficient
- Directly related to the Bandgap voltage (V_{BG})
 - Bandgap voltage is an intrinsic property of a semiconductor
 - It doesn't depend on PVT variation, and this is what we want!
 - Our target is to get this voltage and use that as a way of making a voltage reference!

Idea of BGR

$$V_{BE} = \underbrace{\frac{kT}{q} \ln(I_c)}_{\text{Weak PTAT}} - \underbrace{\frac{kT}{q} \ln(E) - \frac{5 kT}{2 q} \ln(T)}_{\text{Strong CTAT}} + \underbrace{V_{BG}}_{\text{Constant BG voltage}}$$

- Increase “Weak PTAT” to be equal to “Strong CTAT”
 - They will cancel each other!
 - Mathematically: $ZTC(T) = K \cdot PTAT(T) + CTAT(T)$
- We’ll be left with a CONSTANT Bandgap Voltage
 - For Silicon it is approximately 1.2 V

Idea of BGR



$$V_{BE} = \underbrace{\frac{kT}{q} \ln(I_c)}_{\text{Weak PTAT}} - \underbrace{\frac{kT}{q} \ln(E) - \frac{5}{2} \frac{kT}{q} \ln(T)}_{\text{Strong CTAT}} + \underbrace{V_{BG}}_{\text{Constant BG voltage}}$$

$$V_{BE} = \underbrace{\frac{kT}{q} \ln\left(\frac{I_c}{I_s}\right)}_{\text{Weak PTAT}} + \underbrace{\quad}_{\text{Strong CTAT}}$$

- But first of all, We need to extract “Weak PTAT” from V_{BE} !
 - How can we do that?

Choice of N (Making PTAT Stronger)

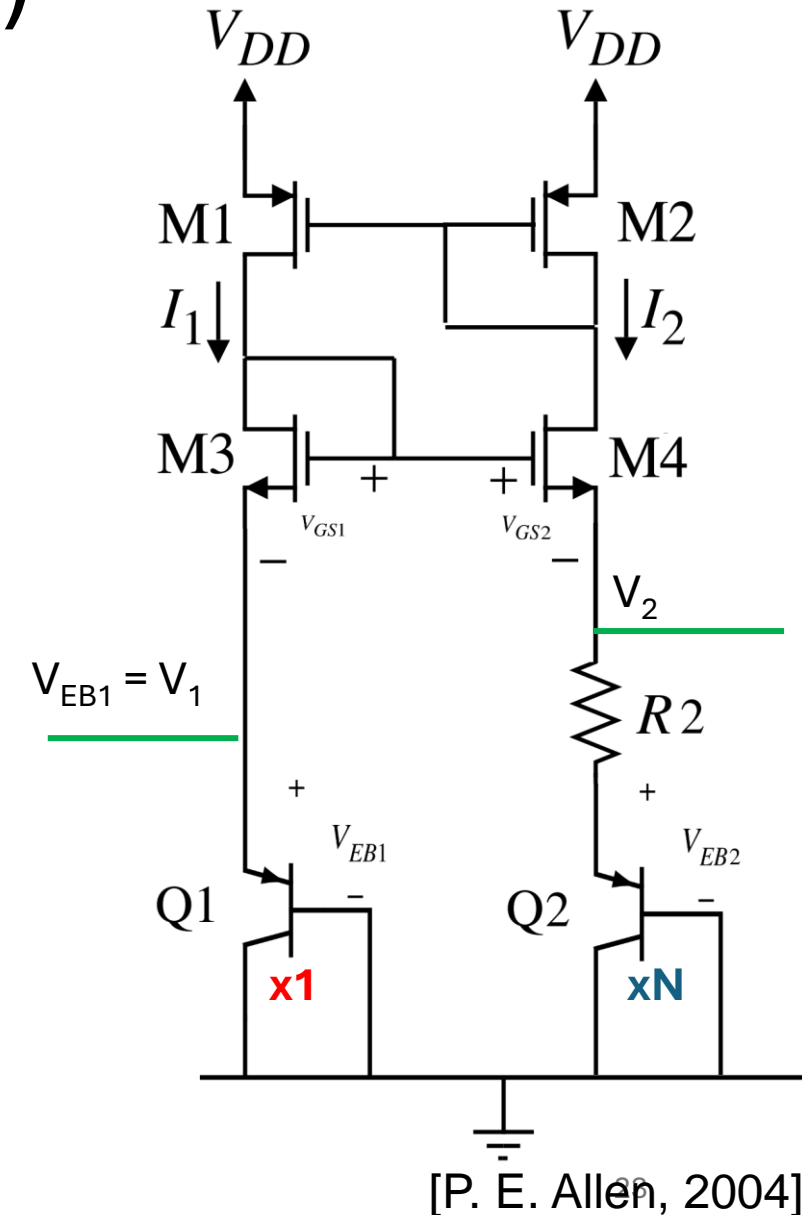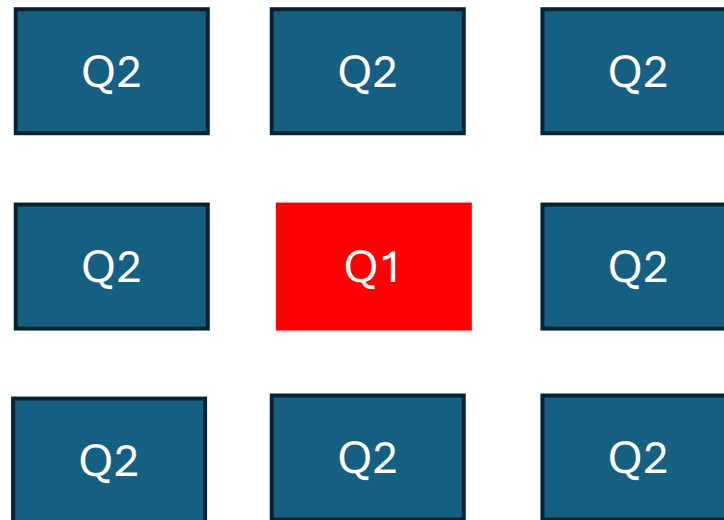- Usually the value of “N” is chosen such a way to make $N = \text{integer}^2 - 1$
- For example, $N = 8$ ($3^2 - 1$)
- Why??
- Because of matching in layout. E.g. Common-centroid matching




Extracting PTAT




- Make $I_1 = I_2 = I$ and $V_1 = V_2$ using current mirror or OpAmp
- $V_{BE1} = RI + V_{BE2}$
- $V_{BE1} - V_{BE2} = RI$
- $\frac{kT}{q} \ln\left(\frac{I_C}{I_S}\right) - \frac{kT}{q} \ln\left(\frac{I_C}{NI_S}\right) = RI$ [Assuming identical BJT]
- $\frac{kT}{q} \ln(N) = RI$
- $I = \frac{kT}{qR} \ln(N)$

PTAP Current



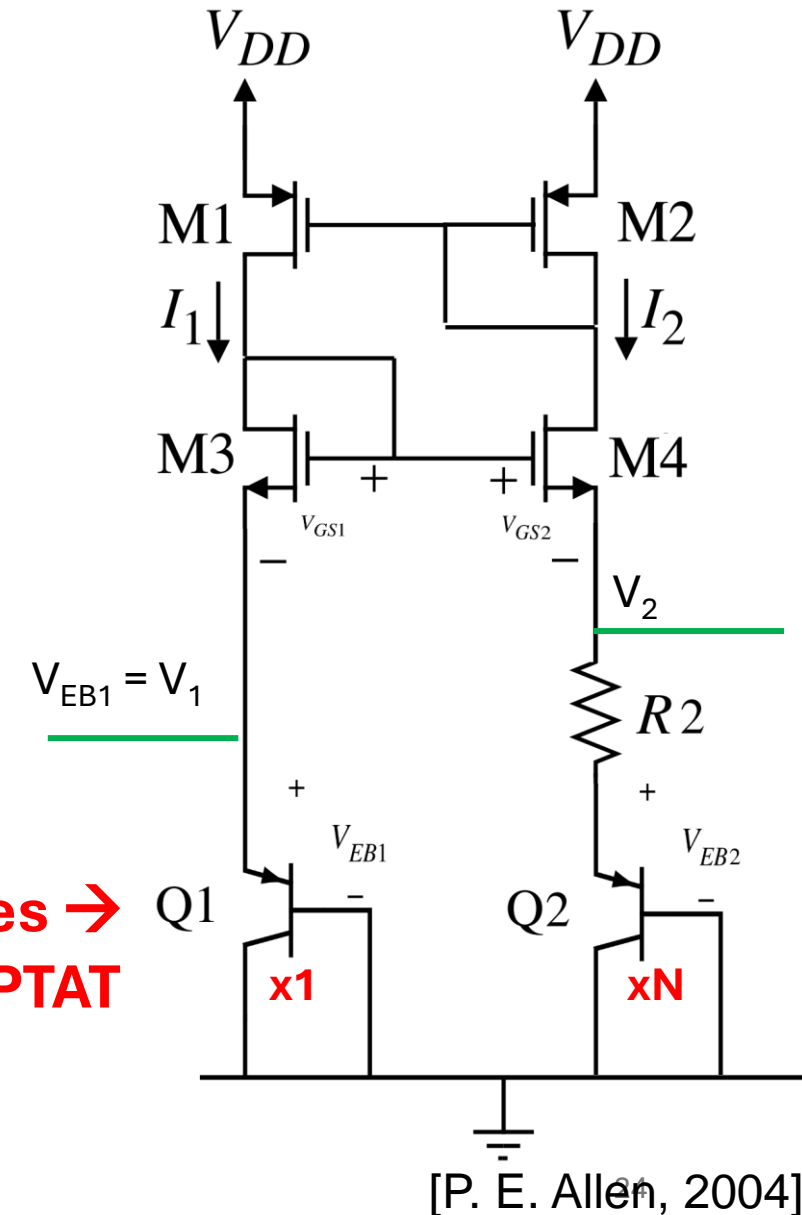
**→ Use CM to generate multiple copies →
Drop it across a resistor to generate PTAT
Voltage**



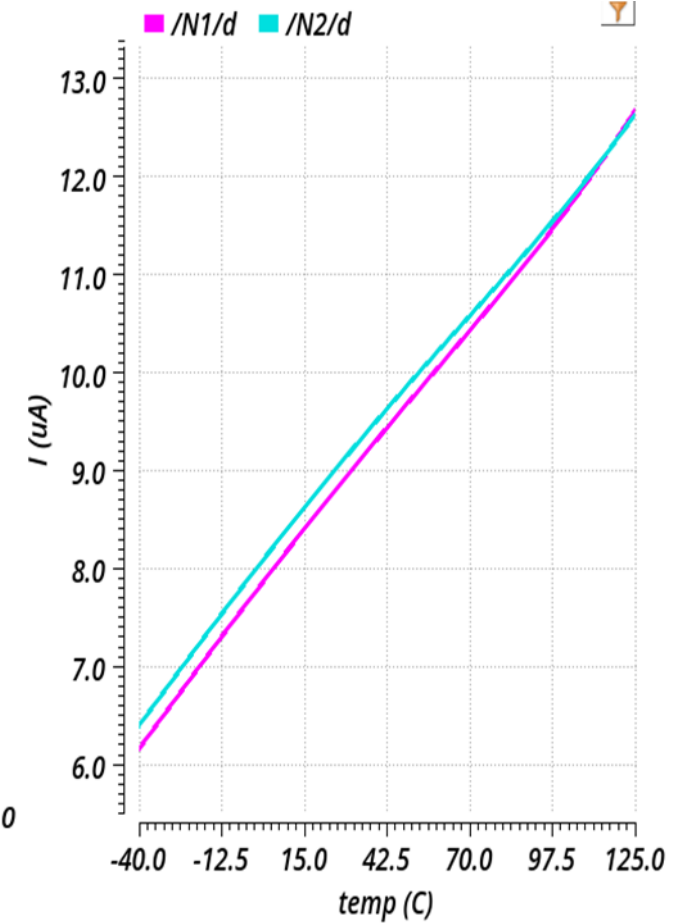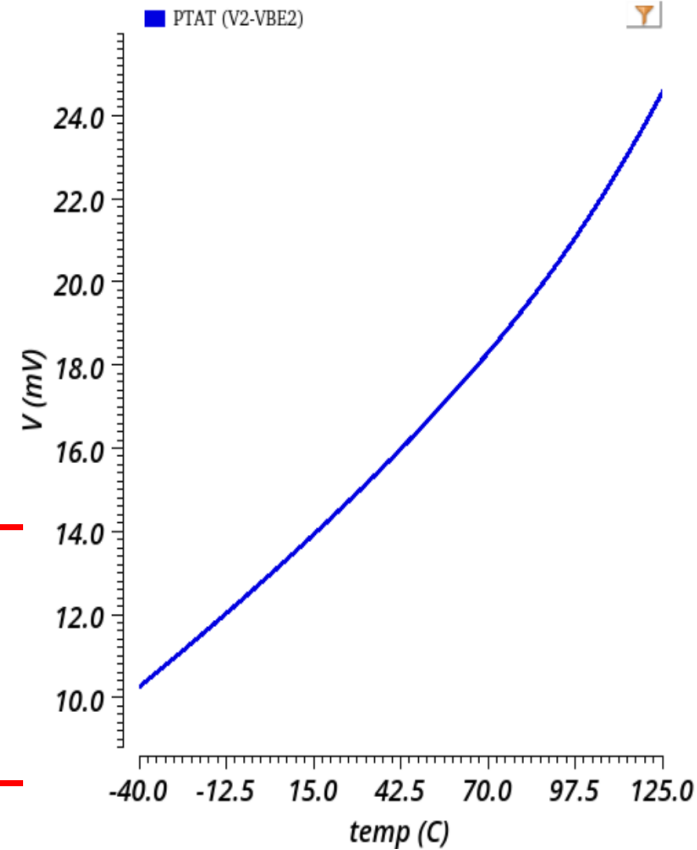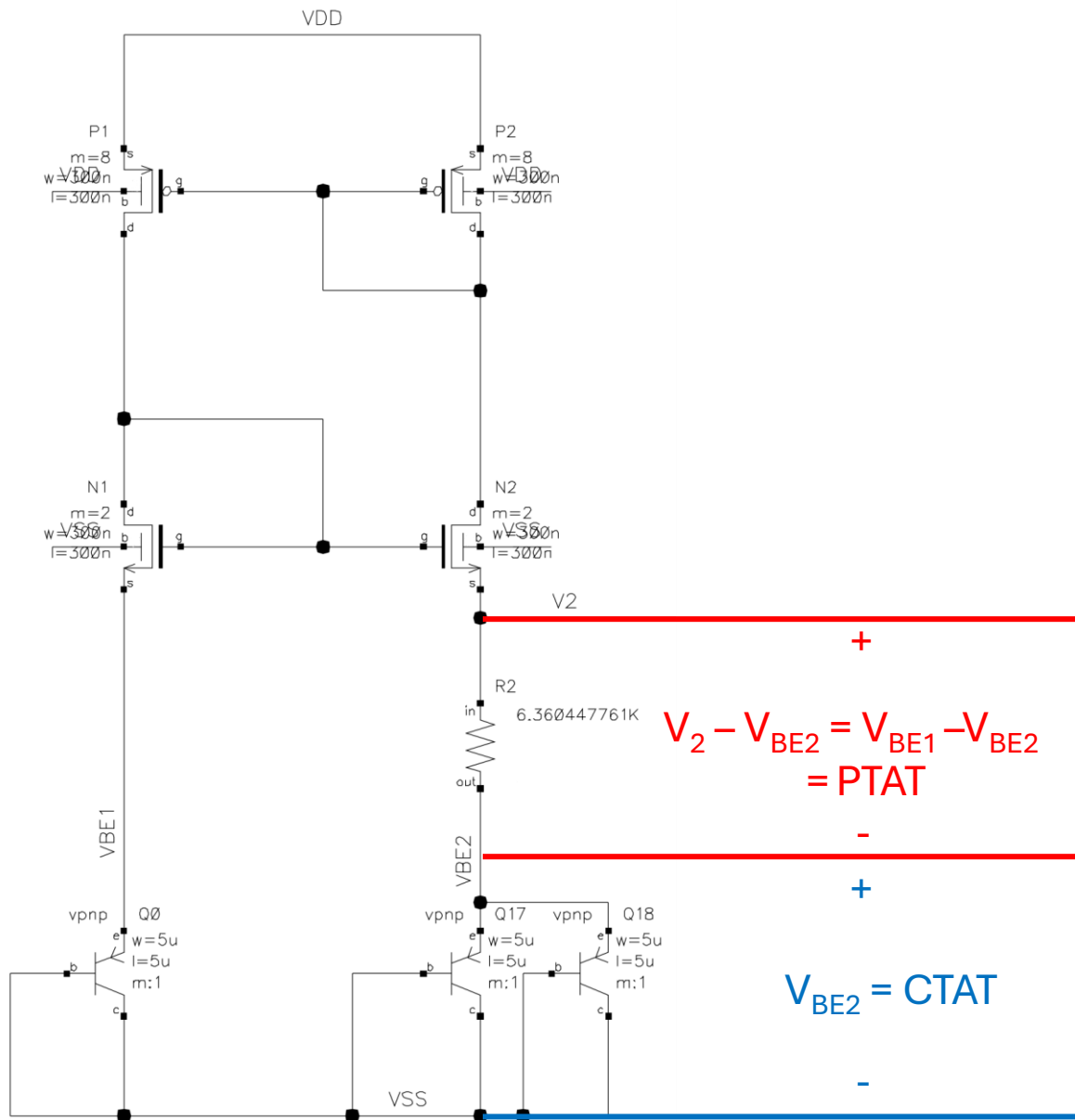Simulation Verification of PTAT Current and Voltage



Review: CTAT

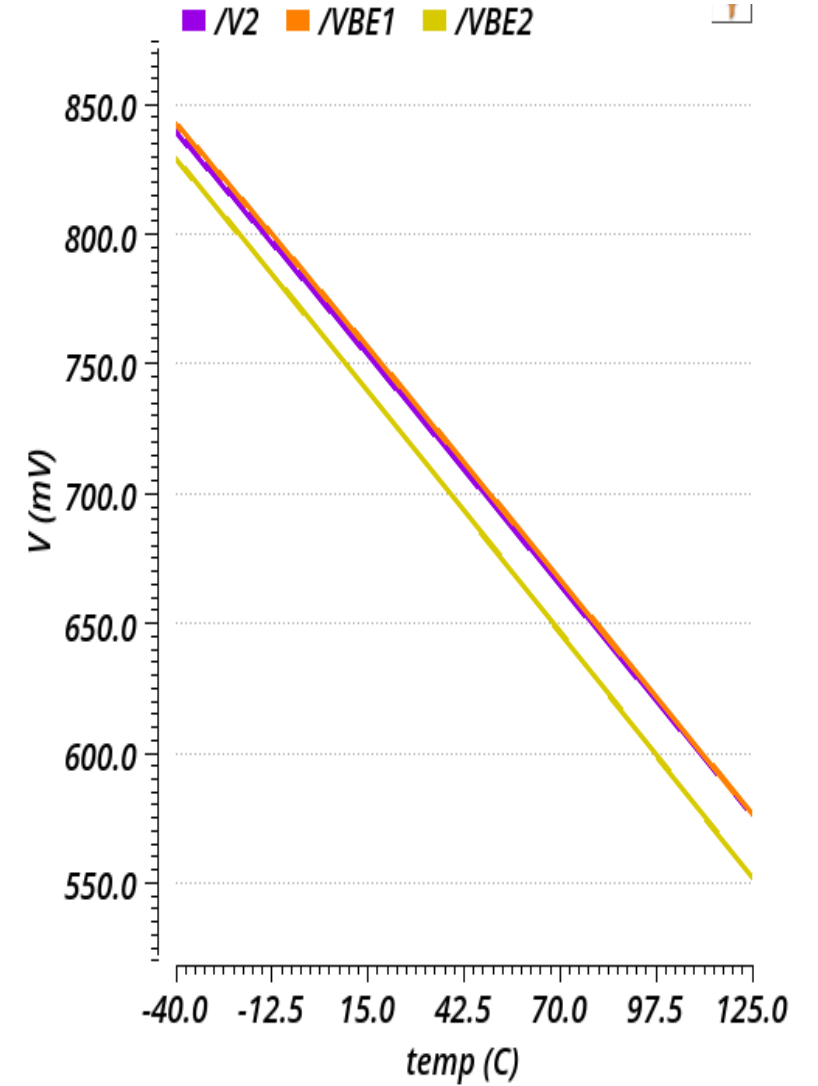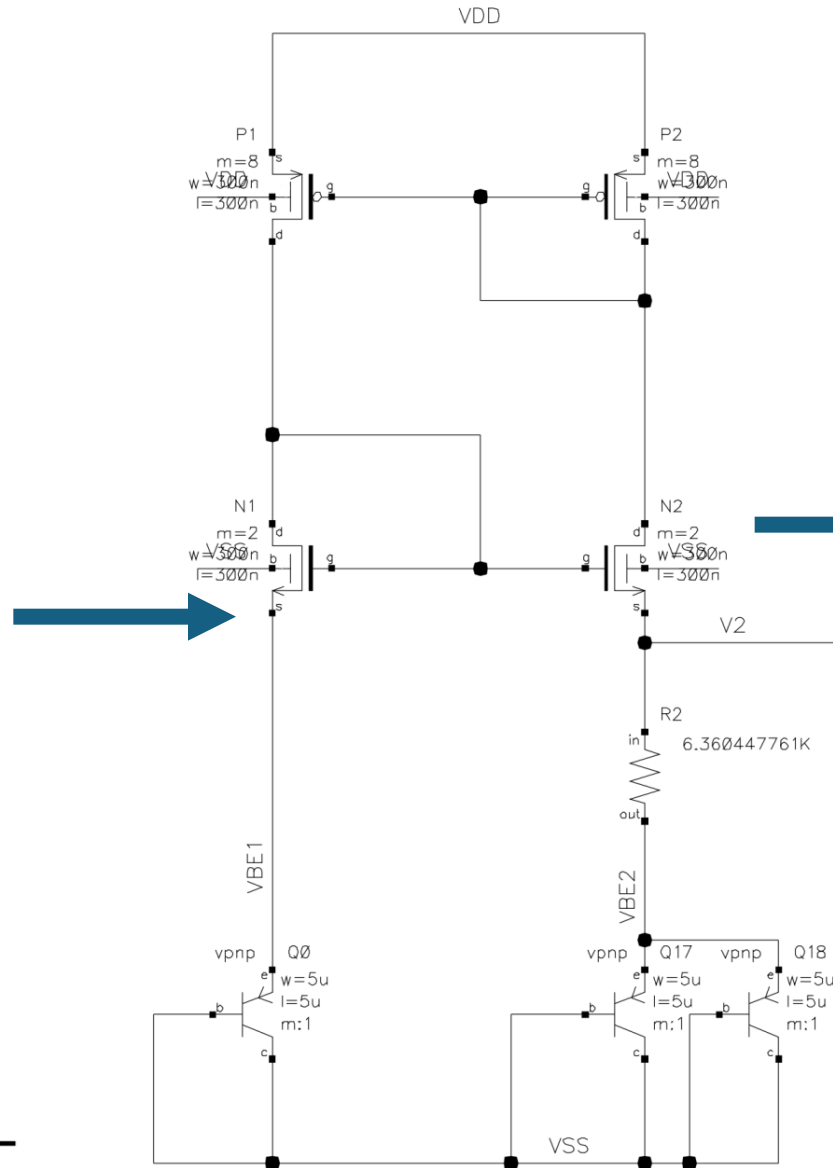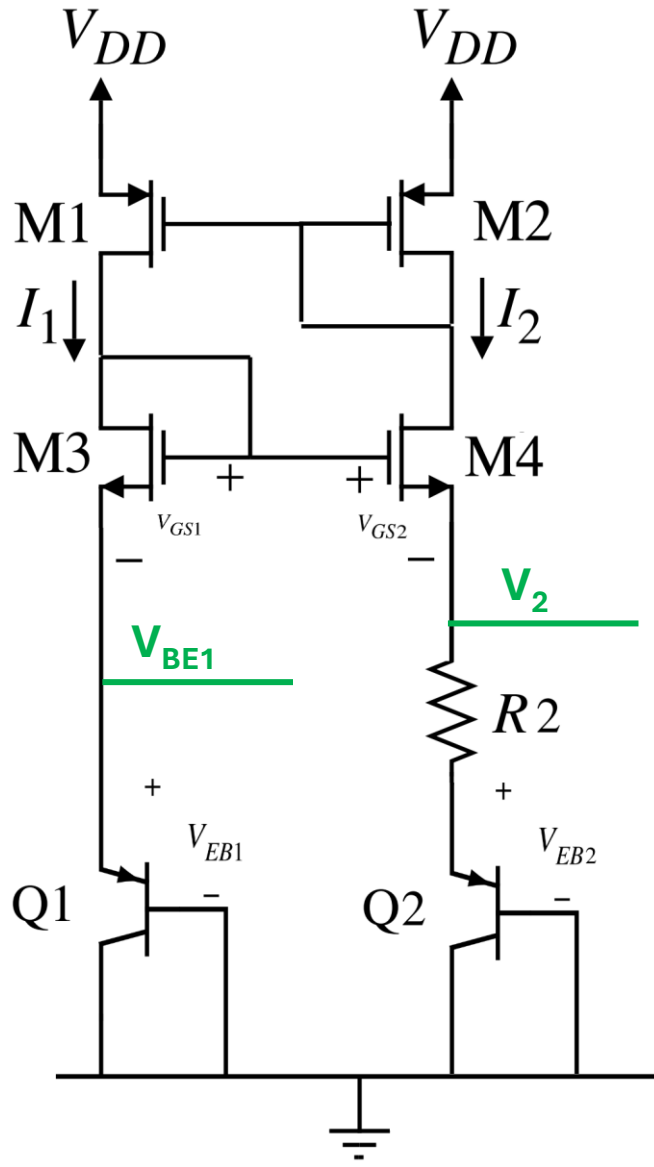


Extracting PTAT Voltage Separately

$$I_{PTAT} = \frac{kT}{qR} \ln(N)$$




PTAP Current

→ Use CM to copy PTAT current

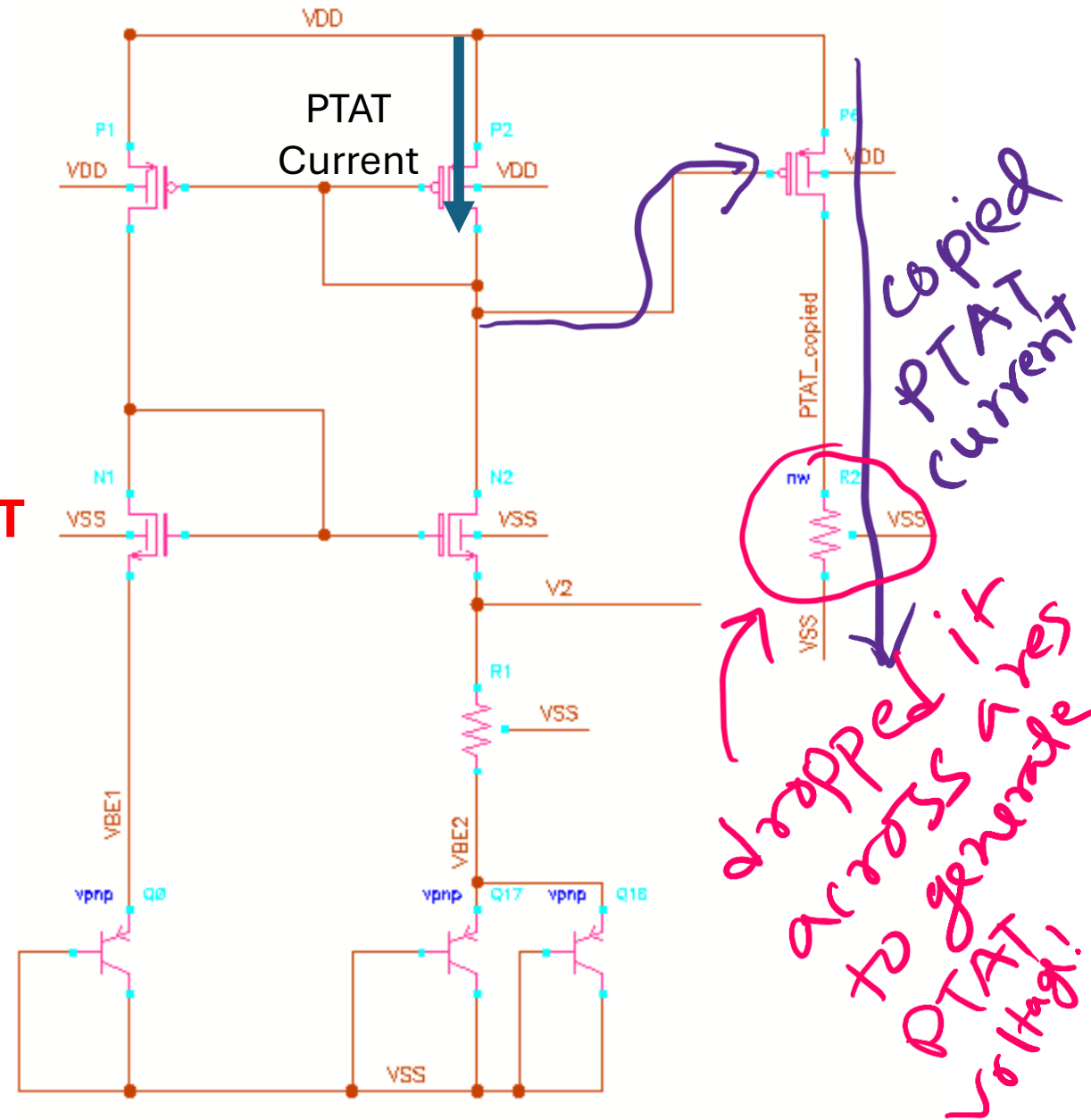→ Drop it across a resistor to generate PTAT Voltage



Extracting PTAT Voltage Separately

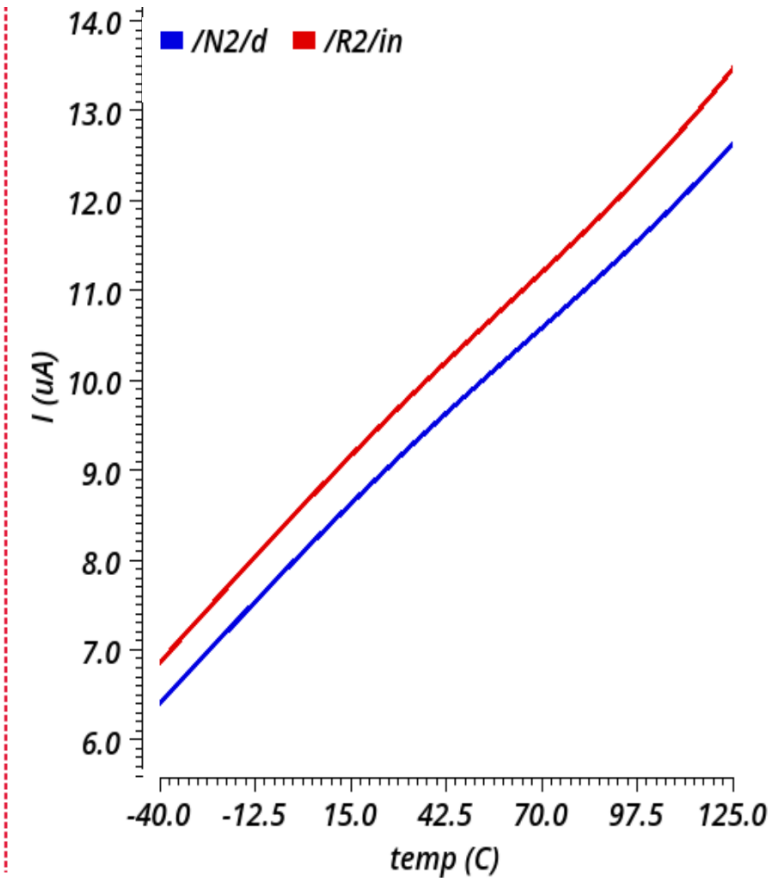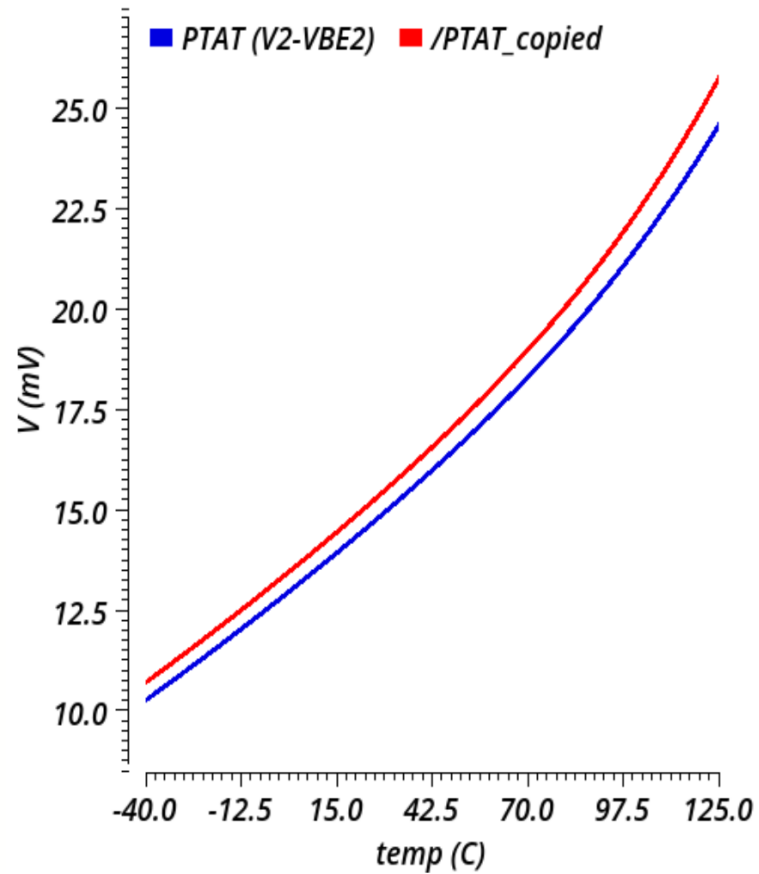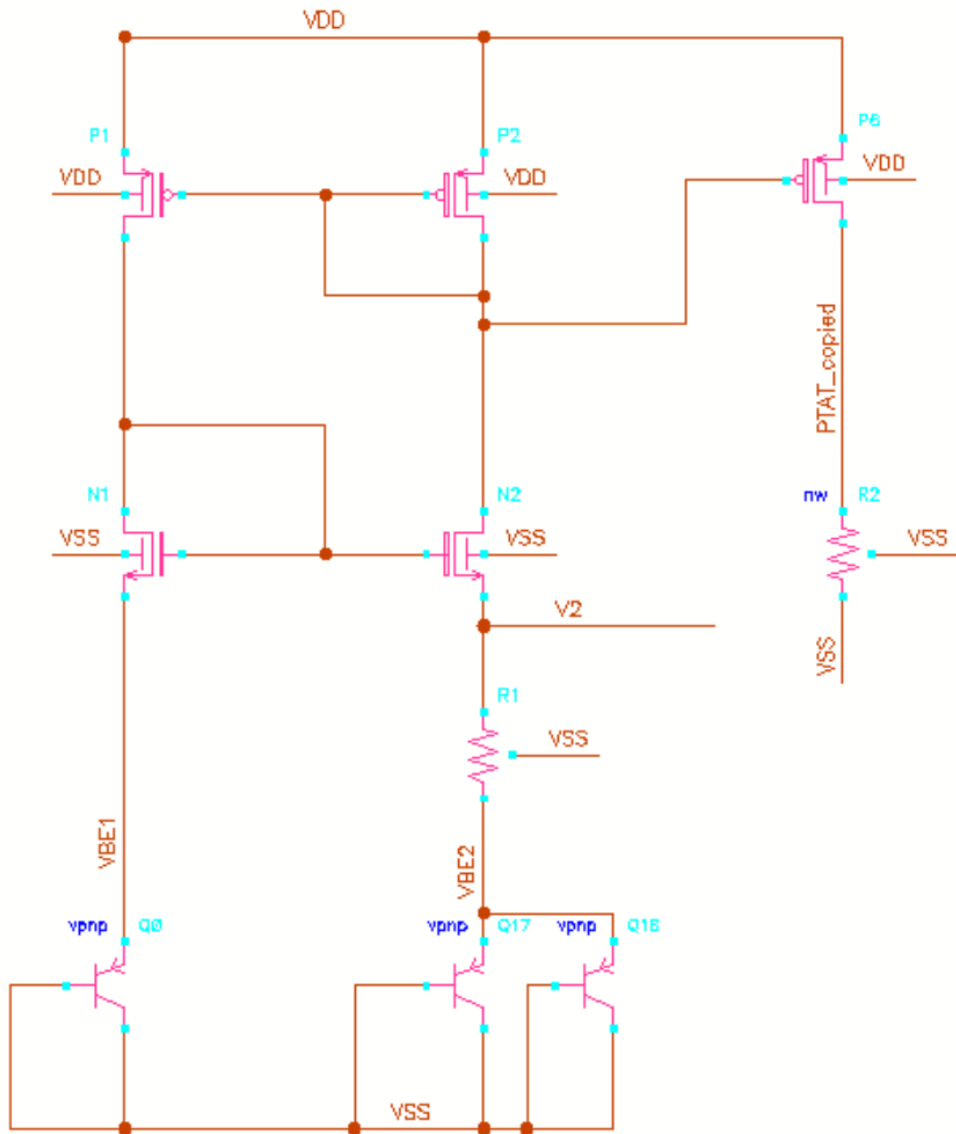


Review: Idea of BGR

$$V_{BE} = \underbrace{\frac{kT}{q} \ln(I_c)}_{\text{Weak PTAT}} - \underbrace{\frac{kT}{q} \ln(E) - \frac{5kT}{2q} \ln(T)}_{\text{Strong CTAT}} + \underbrace{V_{BG}}_{\text{Constant BG voltage}}$$


- Increase “Weak PTAT” to be equal to “Strong CTAT”
 - They will cancel each other!
 - Mathematically
 - $ZTC(T) = K \cdot PTAT(T) + CTAT(T)$
 - $= \frac{R_2}{R_1} \cdot PTAT(T) + CTAT(T)$



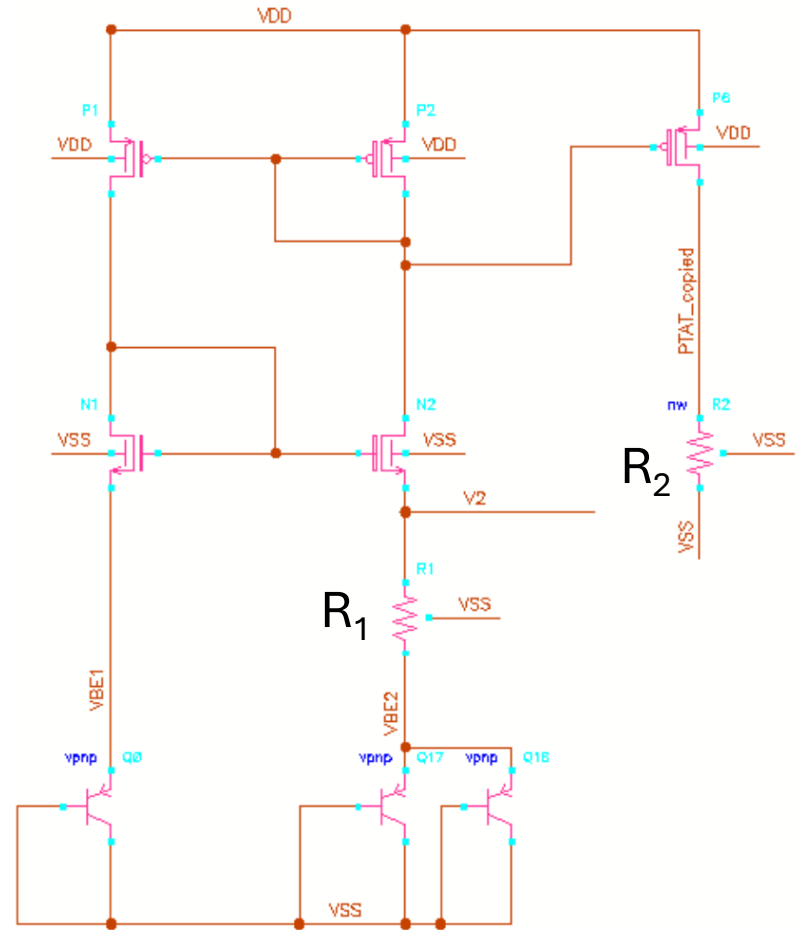
Increase R2/R1 Ratio to make PTAT Stronger



Review: Kirchhoff's Voltage Law (KVL)

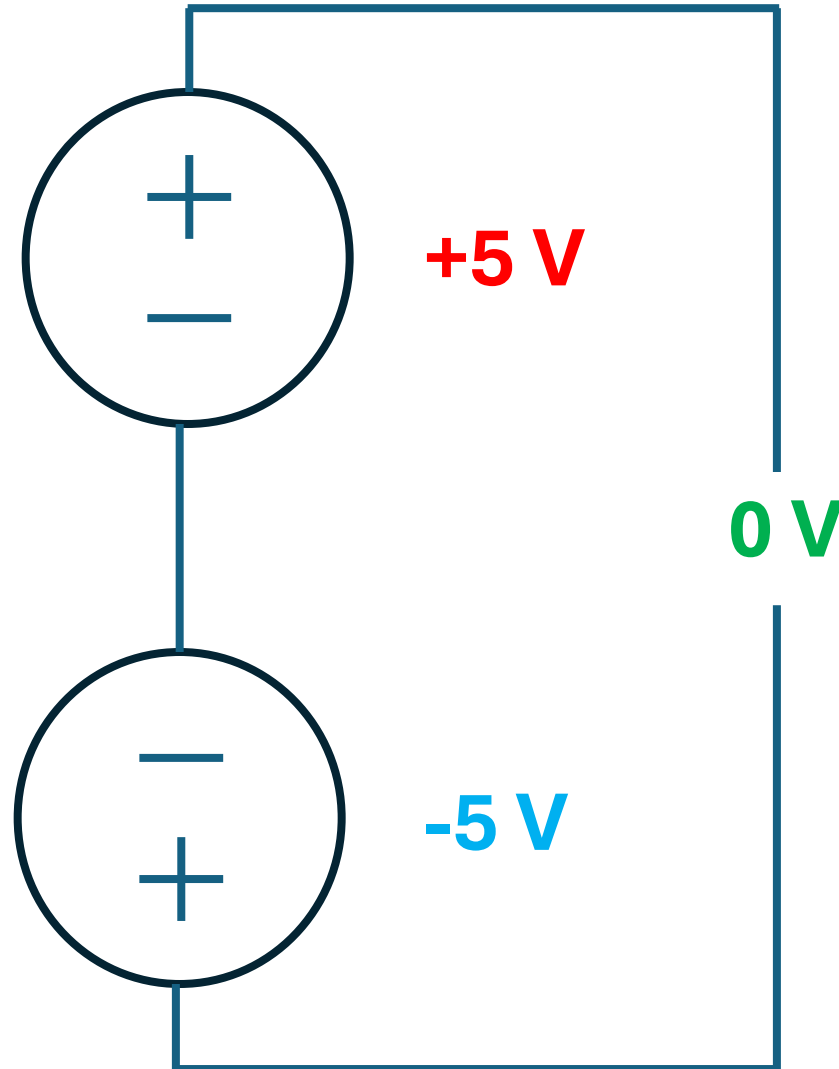


BGR: Apply KVL

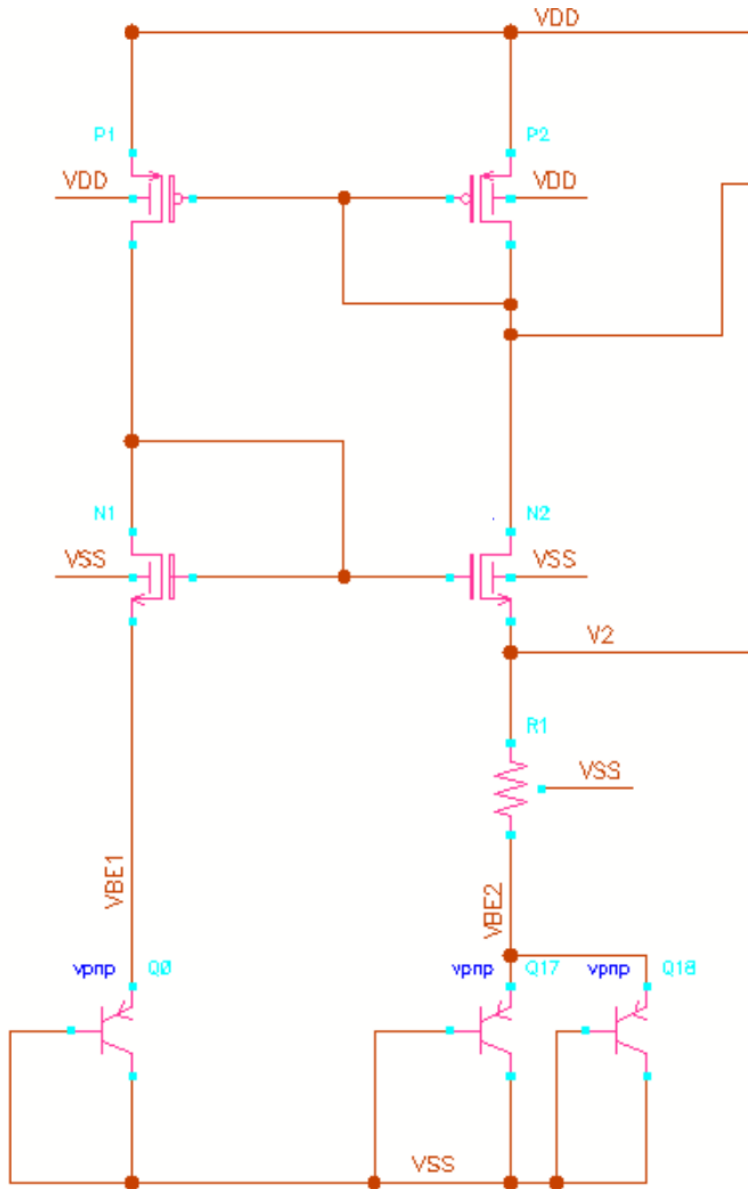



Cancels out each other
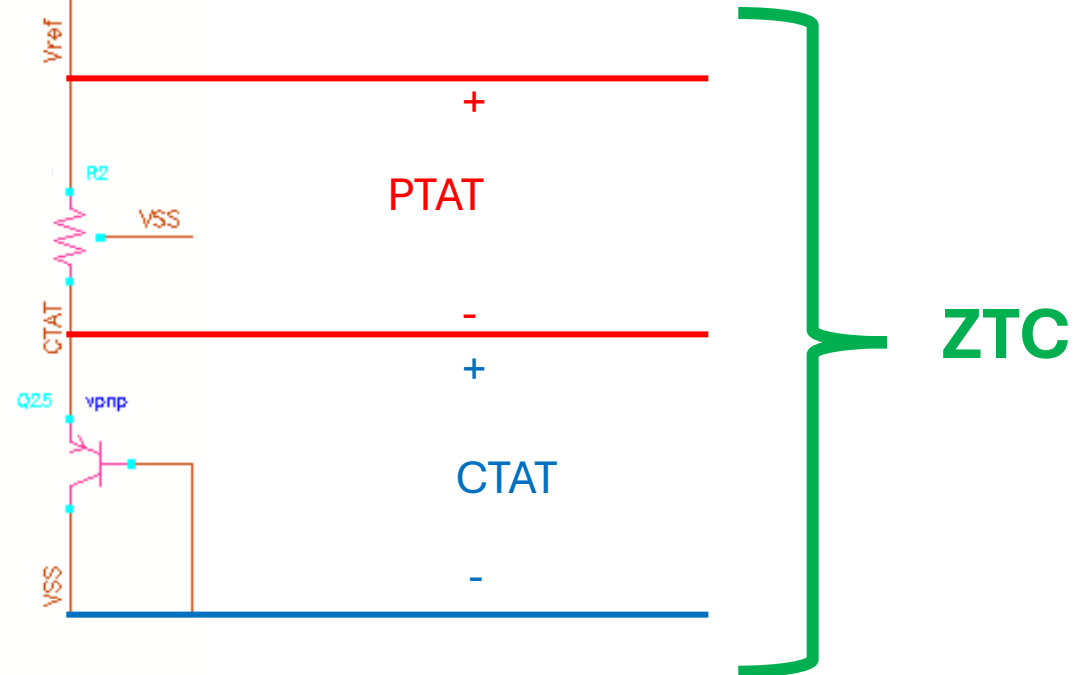
$$V_{ref} = \underbrace{\frac{R_2}{R_1} \cdot \ln(I_c) \frac{kT}{q}}_{\text{Strong PTAT}} - \underbrace{V_{BE}}_{\text{Strong CTAT}} + \underbrace{V_{BG}}_{\text{BG voltage}}$$



Simulation output of BGR

Sweep the temp from -40°C to 125°C

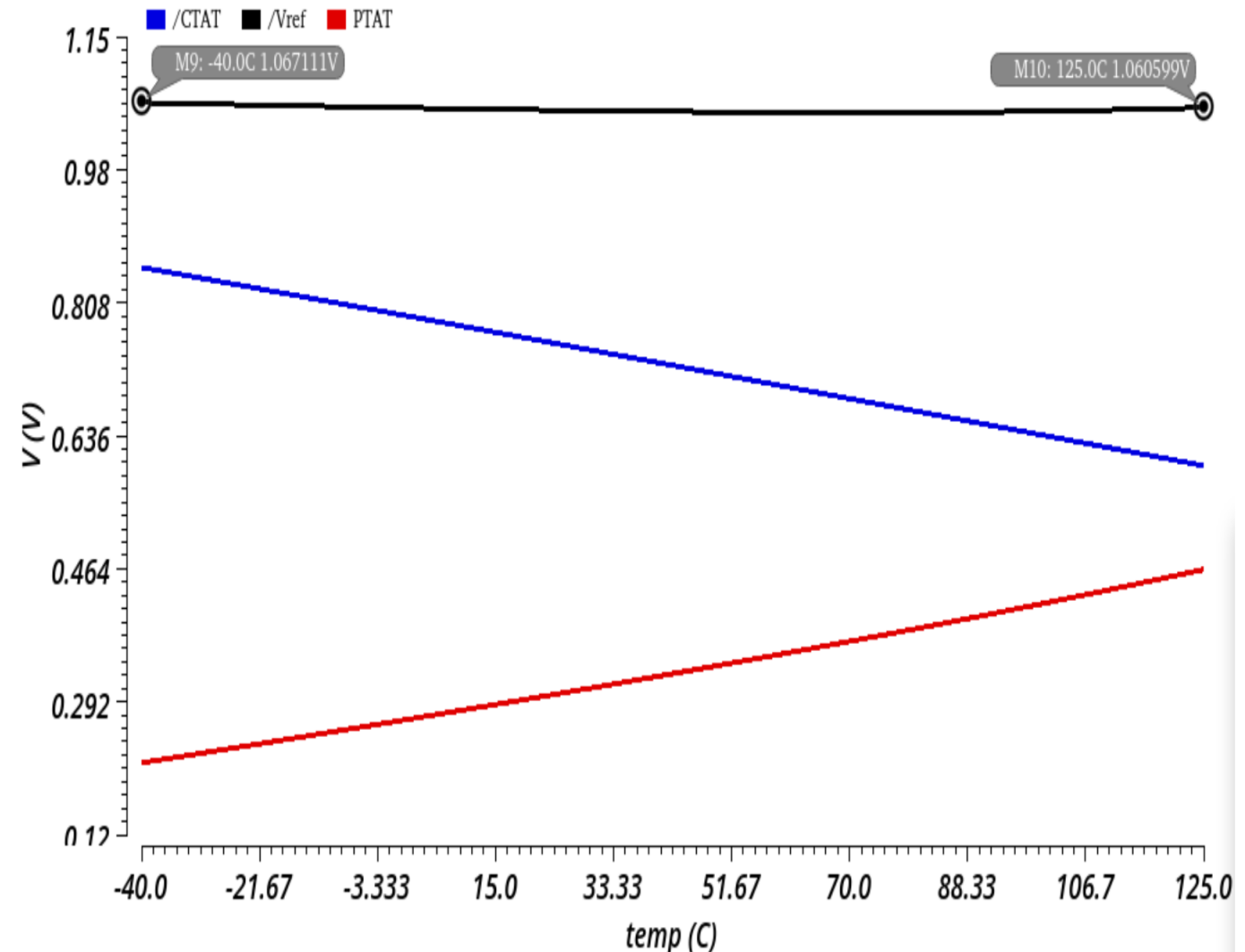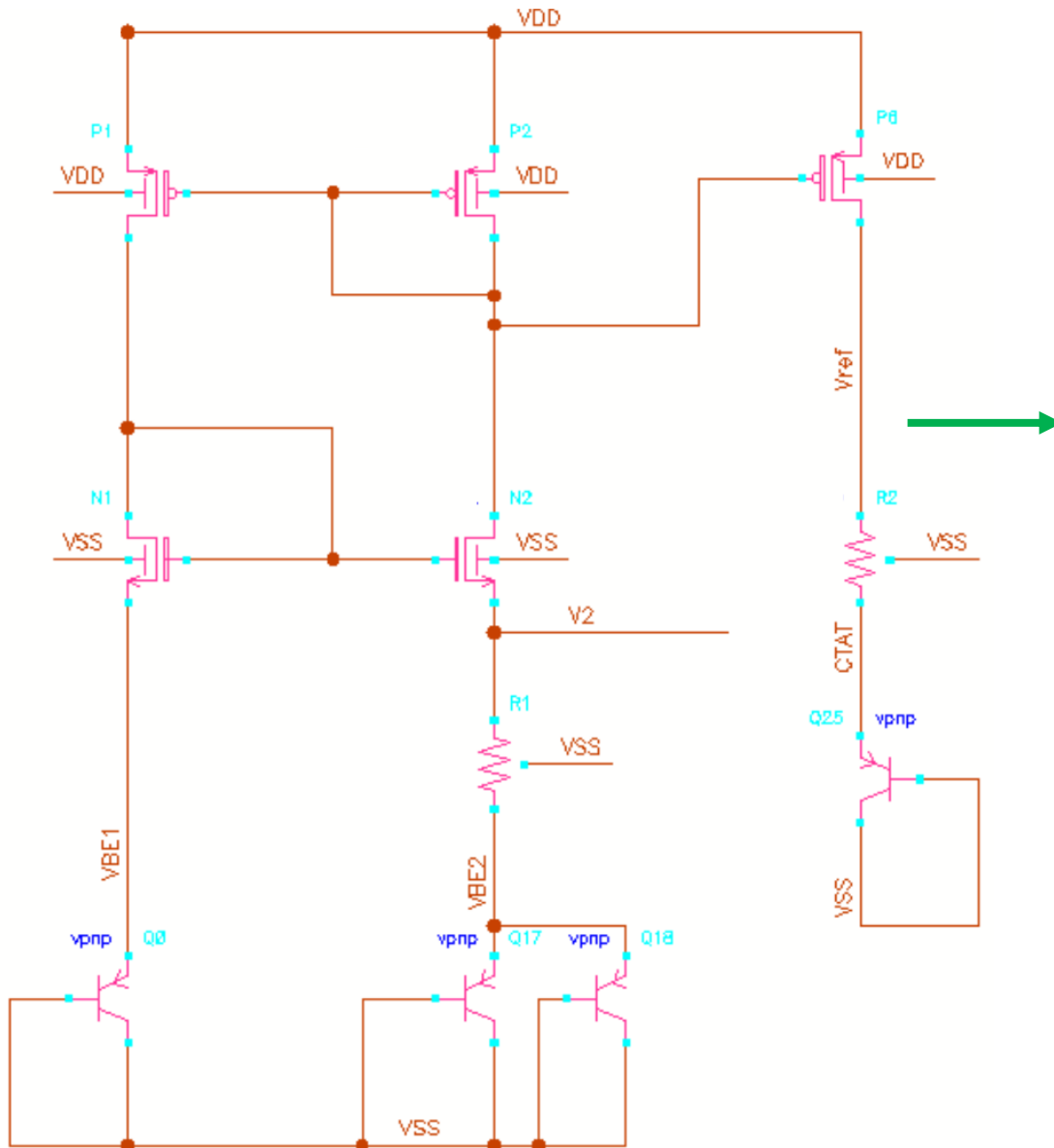

Temperature Coefficient

$$V_{ref_h} = 1.061 \text{ V}$$

$$V_{ref_l} = 1.067 \text{ V}$$

$$T_h = 125^{\circ}\text{C}$$

$$T_l = -40^{\circ}\text{C}$$

$$V_{ref@25C} = 1.060 \text{ V}$$

$$\text{Temp Coefficient} = \frac{|V_{ref_h} - V_{ref_l}|}{T_h - T_l} \times \frac{10^6}{V_{ref@25C}} = \text{ppm}/^{\circ}\text{C}$$

$$\frac{|1.061 - 1.067|}{125 - (-40)} \times \frac{10^6}{1.060} = 34.3 \text{ ppm}/^{\circ}\text{C}$$

The plotted derivative function is


$$\frac{\partial(\text{voltage})}{\partial(\text{temperature})}$$

in units of

$$\frac{\text{V}}{^{\circ}\text{C}}$$

. Divide this function by your nominal Vref - e.g. 1.22V @ 25°C - and multiply it by 1.000.000 (ppm = part per million), so you get

$$\frac{\text{V}}{^{\circ}\text{C}} \times \frac{10^6}{V_{ref}[\text{V}]} = \frac{\text{ppm}}{^{\circ}\text{C}}$$

[kokykokykoky said:](#) 

So which point should I take to be the TC?

The relative temperature dependence of your ref. voltage (in

$$\frac{\text{ppm}}{^{\circ}\text{C}}$$



) will change over the temperature range. Which value you should take depends on your specification needs: you could specify several

$$\frac{\text{ppm}}{^{\circ}\text{C}}$$


values for their corresponding temperature points, or you could specify min. & max values for a specified temperature range, or a mean value for such a range \pm its max. deviations, e.g. for the application temperature range.

See also company bandGap dataSheets how they specify their values.

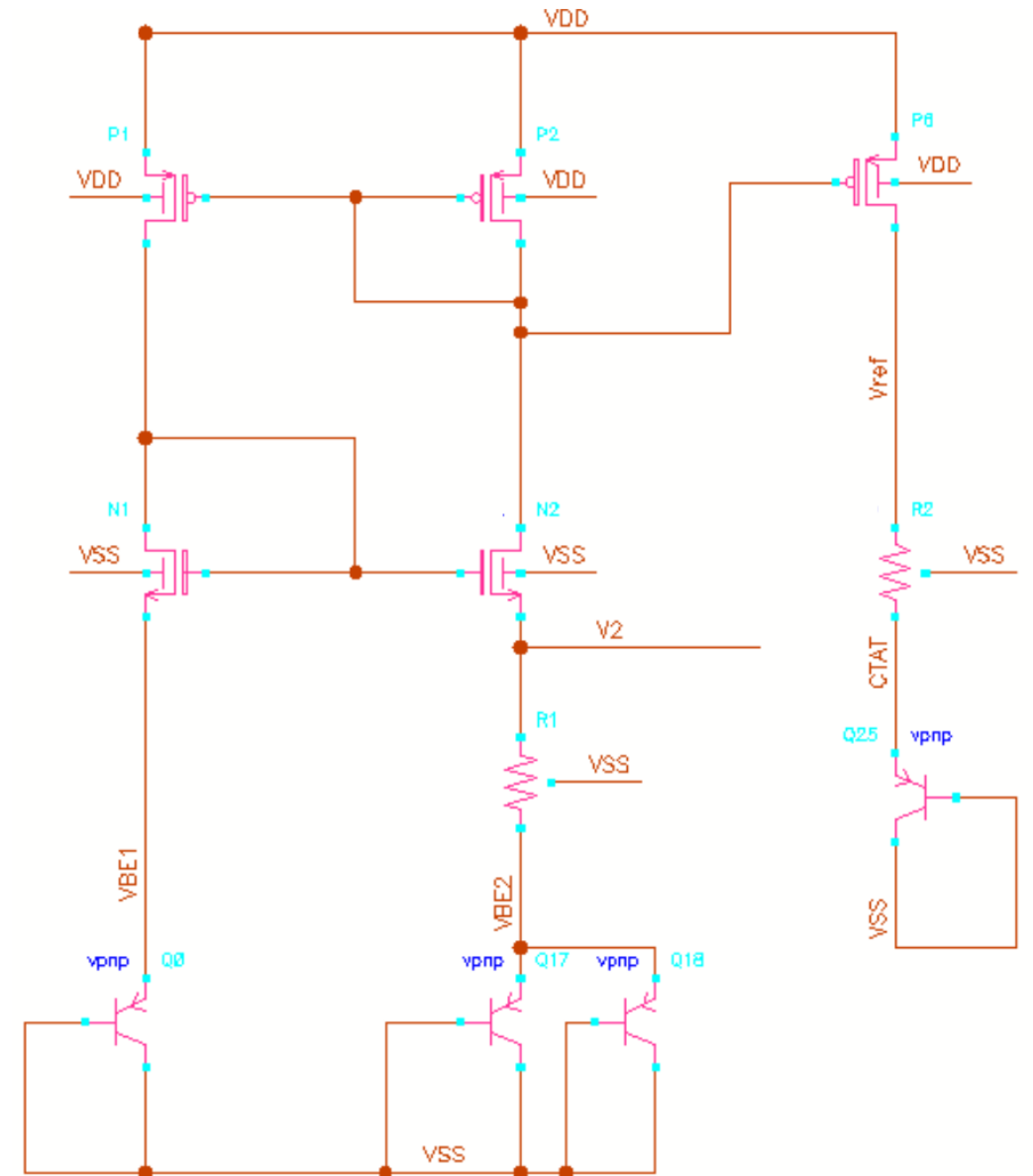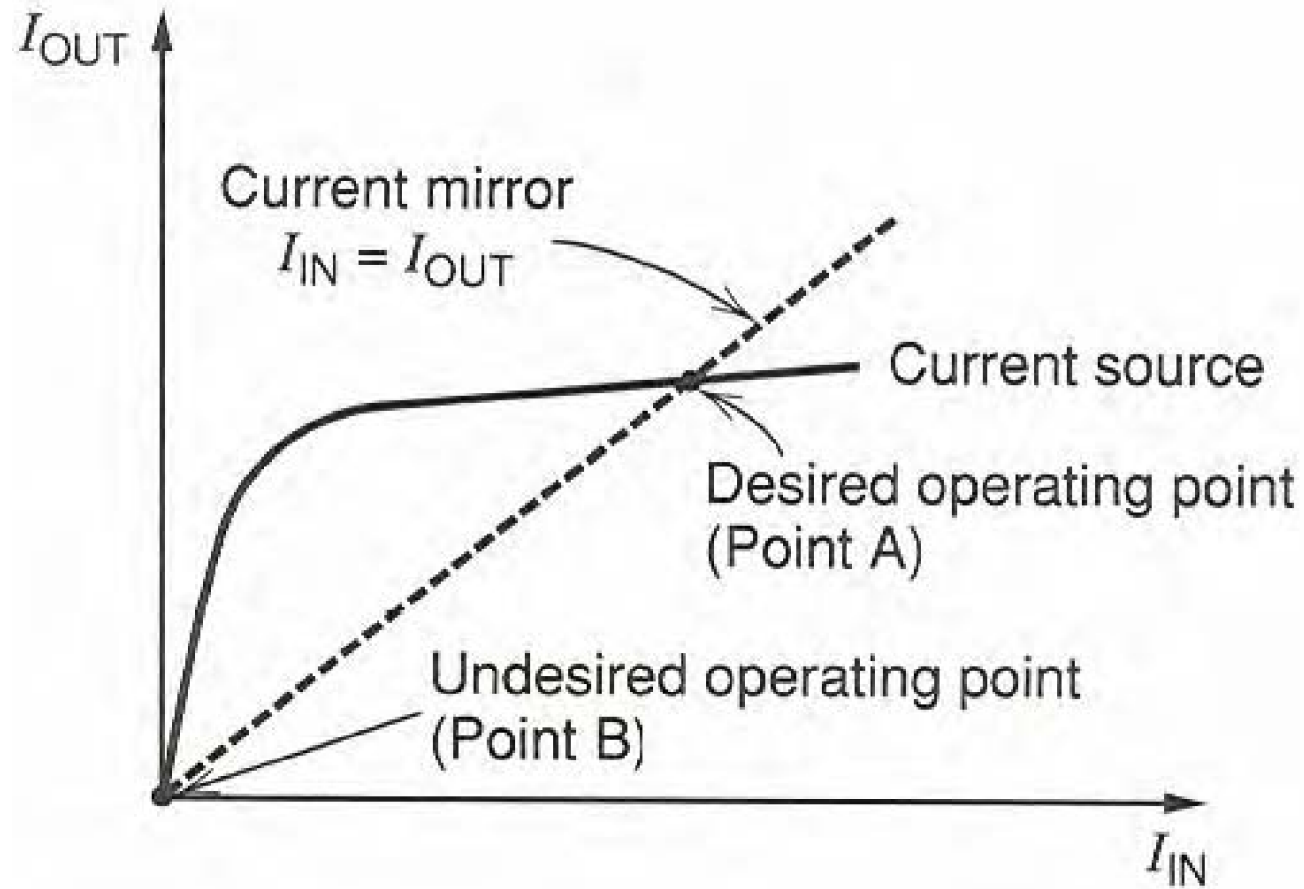Stable Biasing Point of a Reference Source



Start-up Circuit

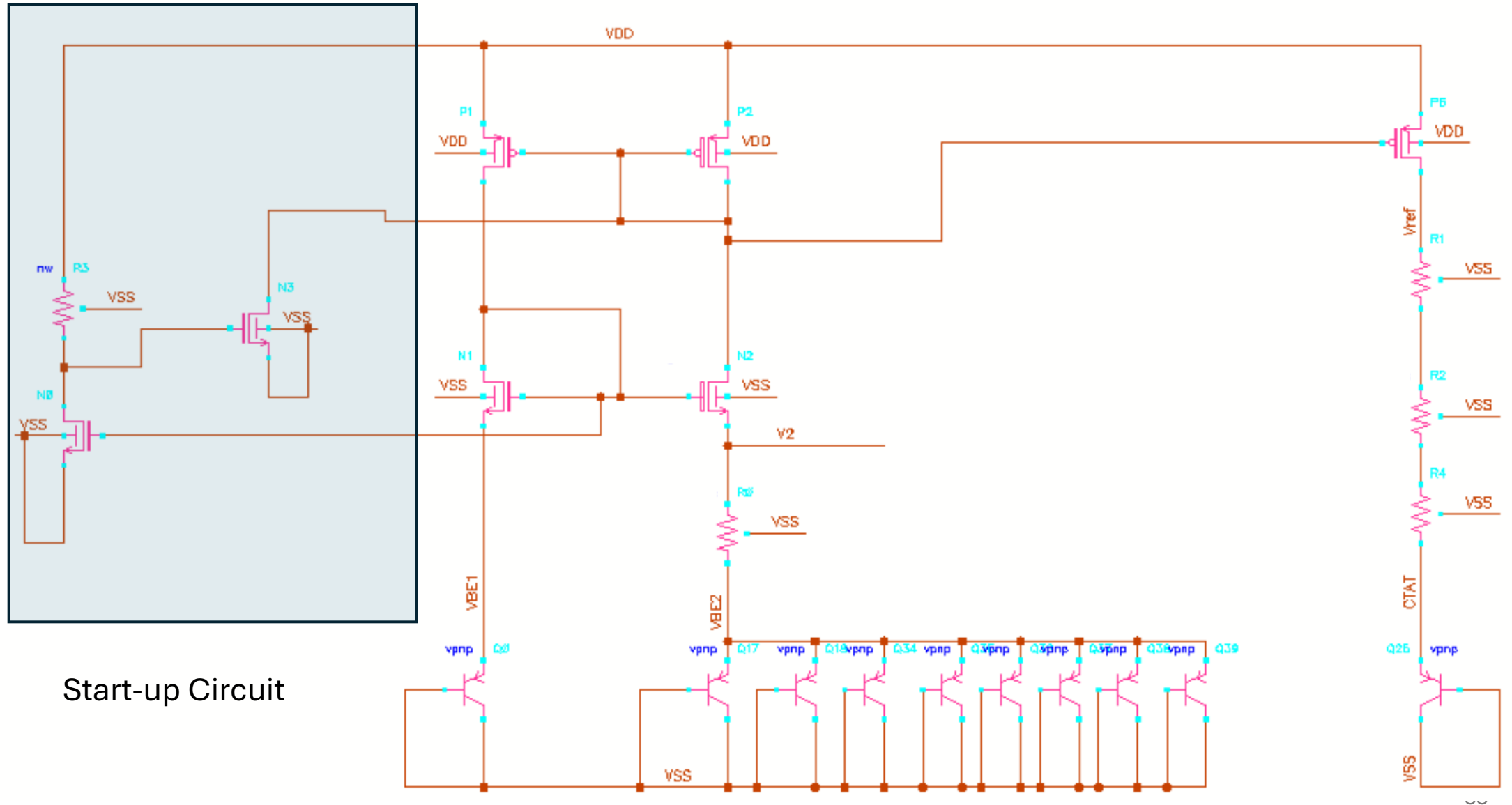

Some good sources for learning more!

- [New Analog Circuit Design \(By Prof. Ali Hajimiri, Caltech\)](#) Lectures 131N to 134N
- [Design of Bandgap Reference](#)

References

- [1] P. E. Allen and D. R. Holberg, "CMOS Analog Circuit Design," 2nd Edition, Oxford University Press, New York, 2004
- [2] Shaheen, Amrozia, Wasif Zia, and Muhammad Sabieh Anwar. "Band structure and electrical conductivity in semiconductors." LUMS School of Science and Engineering, Lahore, Pakistan (2011).
- [3] J. Baker, "Circuit Design, Layout and Simulation", 4th Edition, John Wiley & Sons, July 2019. ISBN 9781119481515

Thank you!