

Shirazush Salekin Chowdhury
Bandgap Reference Circuit

- **PTAT:** One that increases proportionately with temperature and is called proportional to absolute temperature or PTAT. $V_{BE} = \frac{kT}{q} \ln\left(\frac{I_C}{I_S}\right)$
- **CTAT:** One that decreases proportionately with temperature and is called complementary to absolute temperature or CTAT. $V_T = \frac{kT}{q}$

VBE of BJT as CTAT

$$V_{BE} = \frac{kT}{q} \ln\left(\frac{I_C}{I_S}\right)$$

I_S = Saturation Current of BJT

$$I_S = \frac{qA n_i^2 D}{WN_A}$$

Where,

q = Electron Charge (Constant)

A = Area of Emitter (Constant at 1st order)

W = Width of Base (Constant at 1st order)

N_A = Doping Concentration (Constant)

D = Diffusion Constant (NOT CONSTANT)

n_i^2 = Number of intrinsic carrier concentration

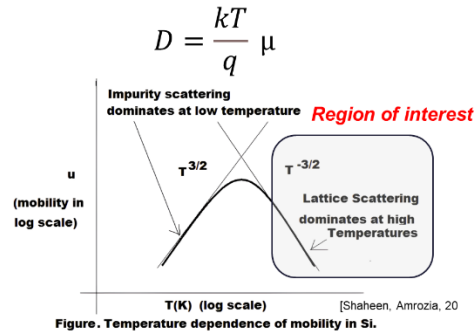


Figure. Temperature dependence of mobility in Si.

$$D = \frac{kT}{q} \mu = \frac{kT}{q} T^{-3/2}$$

$$n_i^2 = D' T^3 e^{-\frac{V_{BG}}{V_T}}$$

$$n_i^2 = D' T^3 e^{-\frac{V_{BG}}{V_T}}$$

$$D = \frac{kT}{q} \mu$$

$$= \frac{kT}{q} T^{-3/2}$$

$$V_{BE} = \frac{kT}{q} \ln\left(\frac{I_C}{I_S}\right)$$

$$I_S = \frac{qA n_i^2 D}{WN_A}$$

$$n_i^2 = D' T^3 e^{-\frac{V_{BG}}{V_T}}$$

$$D = \frac{kT}{q} \mu$$

$$= \frac{kT}{q} T^{-3/2}$$

$$I_S = \frac{qA \left(D' T^3 e^{-\frac{V_{BG}}{V_T}} \right) \frac{kT}{q} T^{-3/2}}{WN_A}$$

$$I_S = E \cdot T^3 \cdot T \cdot T^{-3/2} e^{-\frac{V_{BG}}{V_T}}$$

$$I_S = E \cdot T^{\frac{5}{2}} e^{-\frac{V_{BG}}{V_T}}$$

$$V_{BE} = \frac{kT}{q} \ln(I_C) - \frac{kT}{q} \ln(I_S)$$

$$V_{BE} = \frac{kT}{q} \ln(I_C) - \frac{kT}{q} \ln(E) - \frac{5kT}{2q} \ln(T) + \frac{kT}{q} \cdot \frac{V_{BG}}{V_T}$$

$$V_{BE} = \underbrace{\frac{kT}{q} \ln(I_C)}_{\text{Weak PTAT}} - \underbrace{\frac{kT}{q} \ln(E) - \frac{5kT}{2q} \ln(T)}_{\text{Strong CTAT}} + \underbrace{\frac{kT}{q} \cdot \frac{V_{BG}}{V_T}}_{\text{Constant BG voltage}}$$

Extracting PTAT

- Make $I_1 = I_2 = I$ and $V_1 = V_2$ using current mirror or OpAmp
- $V_{BE1} = RI + V_{BE2}$
- $V_{BE1} - V_{BE2} = RI$
- $\frac{kT}{q} \ln\left(\frac{I_C}{I_S}\right) - \frac{kT}{q} \ln\left(\frac{I_C}{NI_S}\right) = RI$ [Assuming identical BJT] $V_{EB1} = V_1$
- $\frac{kT}{q} \ln(N) = RI$ **PTAP Current**
- $I = \frac{kT}{qR} \ln(N)$ **→ Use CM to generate multiple copies**
→ Drop it across a resistor to generate PTAT Voltage

